

ECE 448

Lecture 9

VHDL Coding for Synthesis

Required reading

- S. Lee, *Advanced Digital Logic Design*,
Chapter 4.4, Synthesis Heuristics (handout)

Non-synthesizable VHDL



High Performance

CoolClock

Low Power

DataCache

Delays

Delays are not synthesizable

Statements, such as

wait for 5 ns

a <= *b* ***after*** 10 ns

*will not produce the required delay, and
should not be used in the code intended
for synthesis.*

Initializations

Declarations of signals (and variables) with initialized values, such as

SIGNAL a : STD_LOGIC := '0';

cannot be synthesized, and thus should be avoided.

If present, they will be ignored by the synthesis tools.

Use set and reset signals instead.

Reports and asserts

Reports and asserts, such as

report "Initialization complete";

assert initial_value <= max_value

report "initial value too large"

severity error;

cannot be synthesized, but they

can be freely used in the code intended for synthesis.

They will be used during simulation and ignored during synthesis.

Floating-point operations

*Operations on signals (and variables)
of the type*

real

*are not synthesizable by the
current generation of synthesis tools.*

Dual-edge flip-flops

```
PROCESS ( Clk )  
BEGIN  
    IF rising_edge(Clk) or falling_edge(CLk) THEN  
        Q <= D ;  
    END IF ;  
END PROCESS ;
```

**Dual-edge flip-flops and registers not synthesizable
using FPGA tools**

Synthesizable VHDL




High Performance

CoolClock


Low Power

DataCache

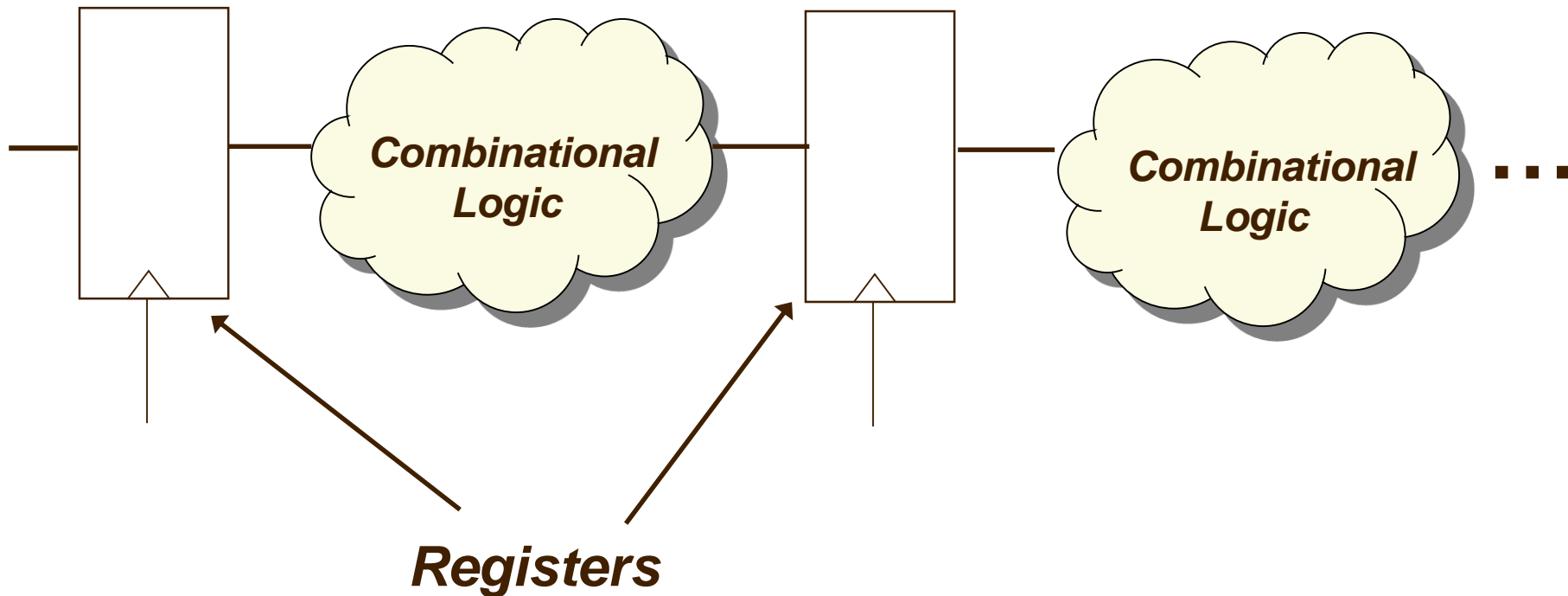Register Transfer Level (RTL) Design Description



VHDL Design Styles

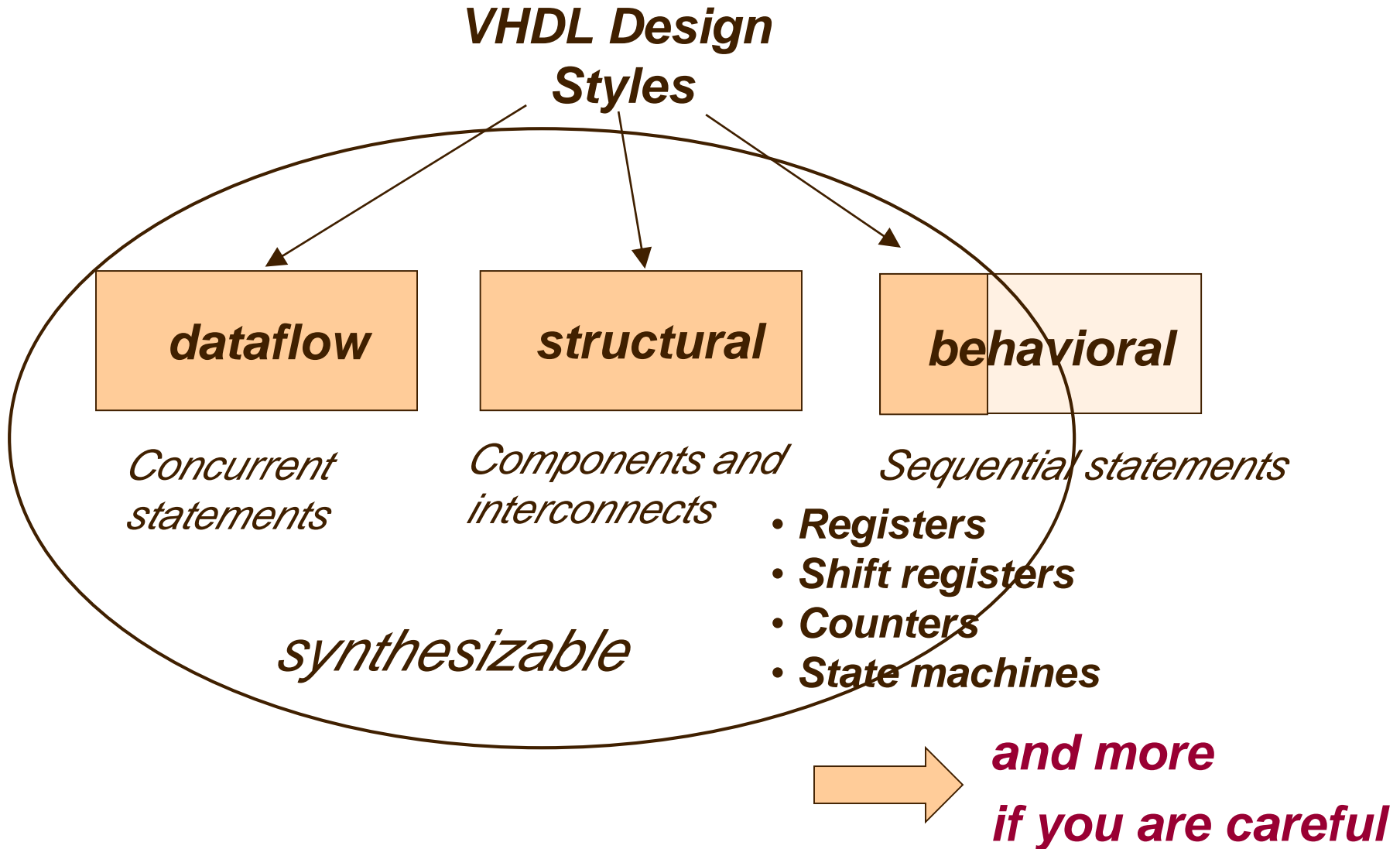

The background is a light blue collage featuring various electronic components and devices. At the top left, a circuit board is shown. To its right is another circuit board. Below the top left board is a mobile phone. In the center, a large integrated circuit (IC) is prominently displayed with the text 'Cooler-II' on it. To the right of the central IC is a keyboard. Below the central IC is another mobile phone. At the bottom right, there is a small electronic component. The background also contains faint, stylized text elements like 'High Performance' and 'Cooler-II'.

Combinational Logic Synthesis for Beginners

Simple rules for beginners

*For combinational logic,
use only concurrent statements*

- *concurrent signal assignment* (\Leftarrow)
- *conditional concurrent signal assignment*
(when-else)
- *selected concurrent signal assignment*
(with-select-when)
- *generate scheme for equations*
(for-generate)

Simple rules for beginners

For circuits composed of

- simple logic operations (logic gates)*
- simple arithmetic operations (addition, subtraction, multiplication)*
- shifts/rotations by a constant*

use

- concurrent signal assignment (\Leftarrow)*

Simple rules for beginners

For circuits composed of

- multiplexers*
- decoders, encoders*
- tri-state buffers*

use

- conditional concurrent signal assignment
(when-else)*
- selected concurrent signal assignment
(with-select-when)*

Left vs. right side of the assignment

Left side

<=

Right side

***<= when-else
with-select <=***

- *Internal signals (defined in a given architecture)*
- *Ports of the mode*
 - **out**
 - *inout*

Expressions including:

- *Internal signals (defined in a given architecture)*
- *Ports of the mode*
 - **in**
 - *inout*

Arithmetic operations

Synthesizable arithmetic operations:

- *Addition, +*
- *Subtraction, -*
- *Comparisons, >, >=, <, <=*
- *Multiplication, **
- *Division by a power of 2, /2**6
(equivalent to right shift)*
- *Shifts by a constant, SHL, SHR*

Arithmetic operations

The result of synthesis of an arithmetic operation is a

- combinational circuit*
- without pipelining.*

*The exact internal **architecture** used (and thus delay and area of the circuit) **may depend** on the **timing constraints** specified during synthesis (e.g., the requested maximum clock frequency).*

Operations on Unsigned Numbers

For operations on unsigned numbers

USE ieee.std_logic_unsigned.all

and

signals (inputs/outputs) of the type

STD_LOGIC_VECTOR

OR

USE ieee.std_logic_arith.all

and

signals (inputs/outputs) of the type

UNSIGNED

Operations on Signed Numbers

For operations on signed numbers

USE ieee.std_logic_signed.all
and
signals (inputs/outputs) of the type
STD_LOGIC_VECTOR

OR

USE ieee.std_logic_arith.all
and
signals (inputs/outputs) of the type
SIGNED

Signed and Unsigned Types

Behave exactly like

STD_LOGIC_VECTOR

plus, they determine whether a given vector should be treated as a signed or unsigned number.

Require

USE ieee.std_logic_arith.all;

Integer Types

*Operations on signals (variables)
of the integer types:*

INTEGER, NATURAL,

and their subtypes, such as

*TYPE day_of_month IS **RANGE 0 TO 31;***

are synthesizable in the range

*$-(2^{31}-1) .. 2^{31}-1$ for **INTEGERs** and their subtypes*

*$0 .. 2^{31}-1$ for **NATURALs** and their subtypes*

Integer Types

*Operations on signals (variables)
of the integer types:*

INTEGER, NATURAL,

*are less flexible and more difficult to control
than operations on signals (variables) of the type*

STD_LOGIC_VECTOR

UNSIGNED

SIGNED, and thus

are recommended to be avoided by beginners.

Addition of Signed Numbers (1)

```
LIBRARY ieee ;  
USE ieee.std_logic_1164.all ;  
USE ieee.std_logic_signed.all ;
```

```
ENTITY adder16 IS  
    PORT ( Cin           : IN      STD_LOGIC ;  
          X, Y           : IN      STD_LOGIC_VECTOR(15 DOWNT0 0) ;  
          S               : OUT     STD_LOGIC_VECTOR(15 DOWNT0 0) ;  
          Cout, Overflow  : OUT     STD_LOGIC ) ;  
END adder16 ;
```

```
ARCHITECTURE Behavior OF adder16 IS  
    SIGNAL Sum : STD_LOGIC_VECTOR(16 DOWNT0 0) ;  
BEGIN  
    Sum <= ('0' & X) + Y + Cin ;  
    S <= Sum(15 DOWNT0 0) ;  
    Cout <= Sum(16) ;  
    Overflow <= Sum(16) XOR X(15) XOR Y(15) XOR Sum(15) ;  
END Behavior ;
```


Addition of Signed Numbers (2)

```
LIBRARY ieee ;
USE ieee.std_logic_1164.all ;
USE ieee.std_logic_arith.all ;

ENTITY adder16 IS
    PORT ( Cin           : IN      STD_LOGIC ;
          X, Y           : IN      SIGNED(15 DOWNT0 0) ;
          S              : OUT     SIGNED(15 DOWNT0 0) ;
          Cout, Overflow : OUT     STD_LOGIC ) ;
END adder16 ;

ARCHITECTURE Behavior OF adder16 IS
    SIGNAL Sum : SIGNED(16 DOWNT0 0) ;
BEGIN
    Sum <= ('0' & X) + Y + Cin ;
    S <= Sum(15 DOWNT0 0) ;
    Cout <= Sum(16) ;
    Overflow <= Sum(16) XOR X(15) XOR Y(15) XOR Sum(15) ;
END Behavior ;
```


Addition of Signed Numbers (3)

```
ENTITY adder16 IS
    PORT ( X, Y      : IN      INTEGER RANGE -32768 TO 32767 ;
           S          : OUT     INTEGER RANGE -32768 TO 32767 ) ;
END adder16 ;
```

```
ARCHITECTURE Behavior OF adder16 IS
BEGIN
    S <= X + Y ;
END Behavior ;
```


Addition of Unsigned Numbers

```
LIBRARY ieee ;
USE ieee.std_logic_1164.all ;
USE ieee.std_logic_unsigned.all ;

ENTITY adder16 IS
    PORT ( Cin           : IN      STD_LOGIC ;
           X, Y          : IN      STD_LOGIC_VECTOR(15 DOWNT0 0) ;
           S             : OUT     STD_LOGIC_VECTOR(15 DOWNT0 0) ;
           Cout          : OUT     STD_LOGIC ) ;
END adder16 ;

ARCHITECTURE Behavior OF adder16 IS
    SIGNAL Sum : STD_LOGIC_VECTOR(16 DOWNT0 0) ;
BEGIN
    Sum <= ('0' & X) + Y + Cin ;
    S <= Sum(15 DOWNT0 0) ;
    Cout <= Sum(16) ;
END Behavior ;
```


Multiplication of signed and unsigned numbers (1)

```
LIBRARY ieee;  
USE ieee.std_logic_1164.all;  
USE ieee.std_logic_arith.all ;
```

```
entity multiply is  
    port(  
        a : in STD_LOGIC_VECTOR(15 downto 0);  
        b : in STD_LOGIC_VECTOR(7 downto 0);  
        cu : out STD_LOGIC_VECTOR(11 downto 0);  
        cs : out STD_LOGIC_VECTOR(11 downto 0)  
    );  
end multiply;
```

architecture dataflow of multiply is

```
SIGNAL sa: SIGNED(15 downto 0);  
SIGNAL sb: SIGNED(7 downto 0);  
SIGNAL sres: SIGNED(23 downto 0);  
SIGNAL sc: SIGNED(11 downto 0);
```

```
SIGNAL ua: UNSIGNED(15 downto 0);  
SIGNAL ub: UNSIGNED(7 downto 0);  
SIGNAL ures: UNSIGNED(23 downto 0);  
SIGNAL uc: UNSIGNED(11 downto 0);
```


Multiplication of signed and unsigned numbers (2)

begin

-- signed multiplication

sa <= SIGNED(a);

sb <= SIGNED(b);

*sres <= sa * sb;*

sc <= sres(11 downto 0);

cs <= STD_LOGIC_VECTOR(sc);

-- unsigned multiplication

ua <= UNSIGNED(a);

ub <= UNSIGNED(b);

*ures <= ua * ub;*

uc <= ures(11 downto 0);

cu <= STD_LOGIC_VECTOR(uc);

end dataflow;

The background is a light blue collage featuring various electronic components and devices. At the top, there are two circular insets showing integrated circuits. Below them, a central square inset shows a microcontroller chip with 'Cooler-II' branding. To the left, a circular inset shows a flip phone, and below it, another shows a mobile phone. To the right, a circular inset shows a keyboard, and below it, another shows a small electronic module. The text 'High Performance' is written in a large, stylized font on the left, and 'CoolerLock' is written in a similar font on the right. The main title is centered in a bold, dark blue font.

Combinational Logic Synthesis for Intermediates

Describing combinational logic using processes

```
LIBRARY ieee ;
USE ieee.std_logic_1164.all ;
ENTITY dec2to4 IS
    PORT ( w      : IN      STD_LOGIC_VECTOR(1 DOWNTO 0) ;
           En     : IN      STD_LOGIC ;
           y      : OUT     STD_LOGIC_VECTOR(0 TO 3) ) ;
END dec2to4 ;

ARCHITECTURE Behavior OF dec2to4 IS
BEGIN
    PROCESS ( w, En )
    BEGIN
        IF En = '1' THEN
            CASE w IS
                WHEN "00" =>          y <= "1000" ;
                WHEN "01" =>          y <= "0100" ;
                WHEN "10" =>          y <= "0010" ;
                WHEN OTHERS =>        y <= "0001" ;
            END CASE ;
            ELSE
                y <= "0000" ;
            END IF ;
        END PROCESS ;
    END Behavior ;
```


Describing combinational logic using processes

```
LIBRARY ieee ;
USE ieee.std_logic_1164.all ;
ENTITY seg7 IS
    PORT ( bcd    : IN      STD_LOGIC_VECTOR(3 DOWNT0 0) ;
          leds    : OUT     STD_LOGIC_VECTOR(1 TO 7) ) ;
END seg7 ;
ARCHITECTURE Behavior OF seg7 IS
BEGIN
    PROCESS ( bcd )
    BEGIN
        CASE bcd IS
            --      abcdefg
            WHEN "0000" => leds <= "1111110" ;
            WHEN "0001" => leds <= "0110000" ;
            WHEN "0010" => leds <= "1101101" ;
            WHEN "0011" => leds <= "1111001" ;
            WHEN "0100" => leds <= "0110011" ;
            WHEN "0101" => leds <= "1011011" ;
            WHEN "0110" => leds <= "1011111" ;
            WHEN "0111" => leds <= "1110000" ;
            WHEN "1000" => leds <= "1111111" ;
            WHEN "1001" => leds <= "1110011" ;
            WHEN OTHERS => leds <= "-----" ;
        END CASE ;
    END PROCESS ;
END Behavior ;
```


Describing combinational logic using processes

```
LIBRARY ieee ;
USE ieee.std_logic_1164.all ;

ENTITY compare1 IS
    PORT ( A, B    : IN    STD_LOGIC ;
           AeqB    : OUT   STD_LOGIC ) ;
END compare1 ;

ARCHITECTURE Behavior OF compare1 IS
BEGIN
    PROCESS ( A, B )
    BEGIN
        AeqB <= '0' ;
        IF A = B THEN
            AeqB <= '1' ;
        END IF ;
    END PROCESS ;
END Behavior ;
```


Incorrect code for combinational logic

- Implied latch (1)


```
LIBRARY ieee ;
USE ieee.std_logic_1164.all ;

ENTITY implied IS
    PORT ( A, B    : IN    STD_LOGIC ;
          AeqB    : OUT   STD_LOGIC ) ;
END implied ;

ARCHITECTURE Behavior OF implied IS
BEGIN
    PROCESS ( A, B )
    BEGIN
        IF A = B THEN
            AeqB <= '1' ;
        END IF ;
    END PROCESS ;
END Behavior ;
```


Incorrect code for combinational logic

- Implied latch (2)

 

Describing combinational logic using processes

Rules that need to be followed:

1. *All inputs to the combinational circuit should be included in the sensitivity list*
2. *No other signals should be included in the sensitivity list*
3. *None of the statements within the process should be sensitive to rising or falling edges*
4. *All possible cases need to be covered in the internal **IF** and **CASE** statements in order to avoid implied latches*

Covering all cases in the IF statement

Using ELSE

```
IF A = B THEN
    AeqB <= '1' ;
ELSE
    AeqB <= '0' ;
```

Using default values

```
AeqB <= '0' ;
IF A = B THEN
    AeqB <= '1' ;
```


Covering all cases in the CASE statement

Using WHEN OTHERS

CASE y IS

WHEN S1 => Z <= "10";

WHEN S2 => Z <= "01";

WHEN OTHERS => Z <= "00";

END CASE;

CASE y IS

WHEN S1 => Z <= "10";

WHEN S2 => Z <= "01";

WHEN S3 => Z <= "00";

WHEN OTHERS => Z <= „--“;

END CASE;

Using default values

Z <= "00";

CASE y IS

WHEN S1 => Z <= "10";

WHEN S2 => Z <= "10";

END CASE;

The background is a light blue collage featuring various electronic components and devices. At the top left, a circuit board is shown. To its right is a microcontroller package. Below these are two circular icons: one showing a computer monitor and keyboard, and another showing a mobile phone. In the center, a large microcontroller package is prominently displayed. To its right is another circular icon showing a keyboard. Below the central package are two more circular icons: one showing a mobile phone and another showing a small electronic component. The text "Sequential Logic Synthesis for Beginners" is overlaid in the center in a bold, dark blue font. The words "High Performance" and "Cooler-11" are also visible in the background, along with other faint text and graphics.

Sequential Logic Synthesis for Beginners

For Beginners

Use processes with very simple structure only to describe

- registers*
- shift registers*
- counters*
- state machines.*

Use examples discussed in class as a template.

*Create **generic** entities for registers, shift registers, and counters, and instantiate the corresponding components in a higher level circuit using GENERIC MAP PORT MAP.*

Supplement sequential components with combinational logic described using concurrent statements.

Sequential Logic Synthesis for Intermediates



For Intermmmediates

1. *Use Processes with IF and CASE statements only. Do not use LOOPS or VARIABLES.*
2. *Sensitivity list of the PROCESS should include **only** signals that can by themsleves change the outputs of the sequential circuit (typically, clock and asynchronous set or reset)*
3. *Do not use PROCESSEs without sensitivity list (they can be synthesizable, but make simulation inefficient)*

For Intermmmediates (2)

Given a single signal, the assignments to this signal should only be made within a single process block in order to avoid possible conflicts in assigning values to this signal.

~~Process 1: PROCESS (a, b)
BEGIN
 y <= a AND b;
END PROCESS;~~

~~Process 2: PROCESS (a, b)
BEGIN
 y <= a OR b;
END PROCESS;~~