

ECE 448

Lecture 3

Combinational-Circuit Building Blocks

Data Flow Modeling of Combinational Logic

Reading

Required

- P. Chu, *FPGA Prototyping by VHDL Examples*
Chapter 3, RT-level combinational circuit

Recommended


- S. Brown and Z. Vranesic, *Fundamentals of Digital Logic with VHDL Design*
Chapter 6, Combinational-Circuit Building Blocks
Chapter 5.5, Design of Arithmetic Circuits Using CAD Tools

Modeling Wires and Buses




Signals


SIGNAL a : STD_LOGIC;

 

SIGNAL b : STD_LOGIC_VECTOR(7 DOWNT0 0);

 


Merging wires and buses

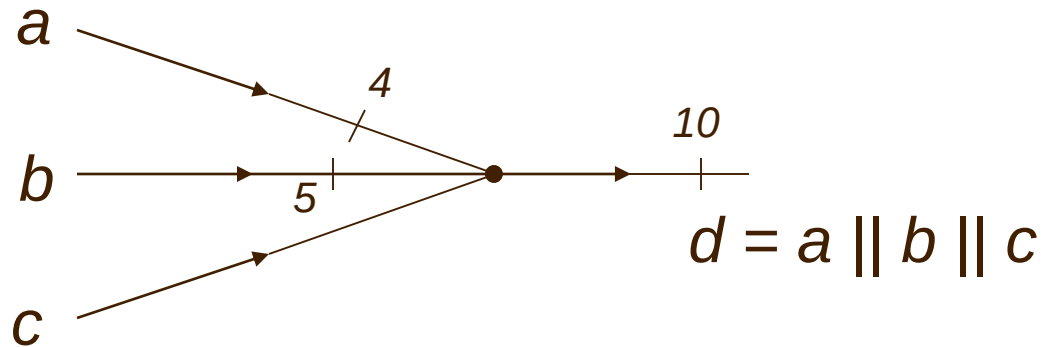

```
SIGNAL a: STD_LOGIC_VECTOR(3 DOWNT0 0);  
SIGNAL b: STD_LOGIC_VECTOR(4 DOWNT0 0);  
SIGNAL c: STD_LOGIC;  
SIGNAL d: STD_LOGIC_VECTOR(9 DOWNT0 0);  
  
d <= a & b & c;
```

Splitting buses

 

```
SIGNAL a: STD_LOGIC_VECTOR(3 DOWNTO 0);  
SIGNAL b: STD_LOGIC_VECTOR(4 DOWNTO 0);  
SIGNAL c: STD_LOGIC;  
SIGNAL d: STD_LOGIC_VECTOR(9 DOWNTO 0);  
  
a <= d(9 downto 6);  
b <= d(5 downto 1);  
c <= d(0);
```



Fixed Shifters & Rotators



Fixed Logical Shift Right in VHDL

SIGNAL A: *STD_LOGIC_VECTOR(3 DOWNT0 0);*

  SIGNAL C: *STD_LOGIC_VECTOR(3 DOWNT0 0);*





C <= '0' & A(3 downto 1);

Fixed Arithmetic Shift Right in VHDL

```
SIGNAL A:   STD_LOGIC_VECTOR(3 DOWNT0 0);
```
  
```
SIGNAL C:   STD_LOGIC_VECTOR(3 DOWNT0 0);
```





$C = A(3) \& A(3 \text{ downto } 1);$

Fixed Logical Shift Left in VHDL

```
SIGNAL A:   STD_LOGIC_VECTOR(3 DOWNT0 0);
```

 
 
```
SIGNAL C:   STD_LOGIC_VECTOR(3 DOWNT0 0);
```



$C = A(2 \text{ downto } 0) \& '0';$

Fixed Rotation Left in VHDL
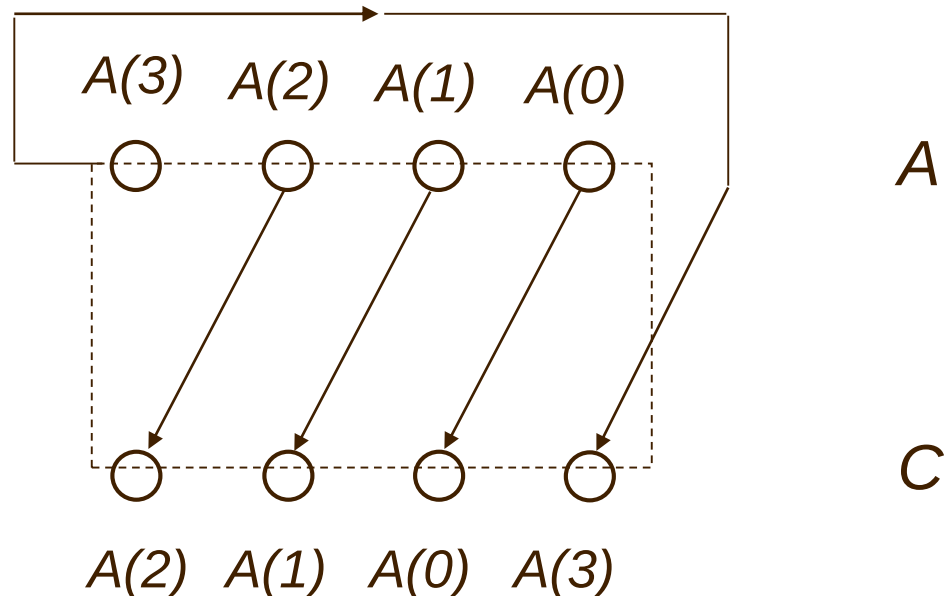 
```
SIGNAL A:   STD_LOGIC_VECTOR(3 DOWNTO 0);  
SIGNAL C:   STD_LOGIC_VECTOR(3 DOWNTO 0);
```



$C = A(2 \text{ downto } 0) \& A(3);$

No Implied Precedence

Wanted: $y = ab + cd$

Incorrect

$y \leq a \text{ and } b \text{ or } c \text{ and } d ;$

equivalent to

$y \leq ((a \text{ and } b) \text{ or } c) \text{ and } d ;$


equivalent to

$y = (ab + c)d$

Correct

$y \leq (a \text{ and } b) \text{ or } (c \text{ and } d) ;$

Cascade of two multiplexers

 

VHDL:

```
y <= w1 WHEN s1 = '1' ELSE  
    w2 WHEN s2 = '1' ELSE  
    w3 ;
```

Priority of logic and relational operators

compare $a = bc$

Incorrect

... when $a = b$ **and** c else ...


equivalent to

... when $(a = b)$ **and** c else ...

Correct

... when $a = (b$ **and** $c)$ else ...

Priority Encoder

 

```
y <= "11" WHEN w(3) = '1' ELSE
      "10" WHEN w(2) = '1' ELSE
      "01" WHEN w(1) = '1' ELSE
      "00" ;
```

```
z <= '0' WHEN w = "0000" ELSE '1' ;
```

w_3	w_2	w_1	w_0	y_1	y_0	z
0	0	0	0	-	-	0
0	0	0	1	0	0	1
0	0	1	-	0	1	1
0	1	-	-	1	0	1
1	-	-	-	1	1	1

VHDL code for a Priority Encoder entity

```
LIBRARY ieee ;
USE ieee.std_logic_1164.all ;

ENTITY priority IS
    PORT ( w   : IN      STD_LOGIC_VECTOR(3 DOWNT0 0) ;
          y   : OUT     STD_LOGIC_VECTOR(1 DOWNT0 0) ;
          z   : OUT     STD_LOGIC ) ;
END priority ;

ARCHITECTURE dataflow OF priority IS
BEGIN
    y <=  "11" WHEN w(3) = '1' ELSE
          "10" WHEN w(2) = '1' ELSE
          "01" WHEN w(1) = '1' ELSE
          "00" ;
    z <=  '0' WHEN w = "0000" ELSE '1' ;
END dataflow ;
```


Adders



High Performance


CoolClock

Low Power

DataCatcher



Adder mod 2^{16}

 

VHDL code for an Adder mod 2^{16}

```
LIBRARY ieee ;
USE ieee.std_logic_1164.all ;
USE ieee.numeric_std.all ;

ENTITY adder16 IS
    PORT (  X          : IN    STD_LOGIC_VECTOR(15 DOWNTO 0) ;
           Y          : IN    STD_LOGIC_VECTOR(15 DOWNTO 0) ;
           S          : OUT   STD_LOGIC_VECTOR(15 DOWNTO 0) ) ;
END adder16 ;

ARCHITECTURE dataflow OF adder16 IS
BEGIN
    S <= std_logic_vector(unsigned(X) + unsigned(Y));
END dataflow ;
```

Signed and Unsigned Types

Behave *exactly like*


STD_LOGIC_VECTOR

plus, they determine whether a given vector should be treated as a signed or unsigned number.

Require

USE ieee.numeric_std.all;

16-bit Unsigned Adder

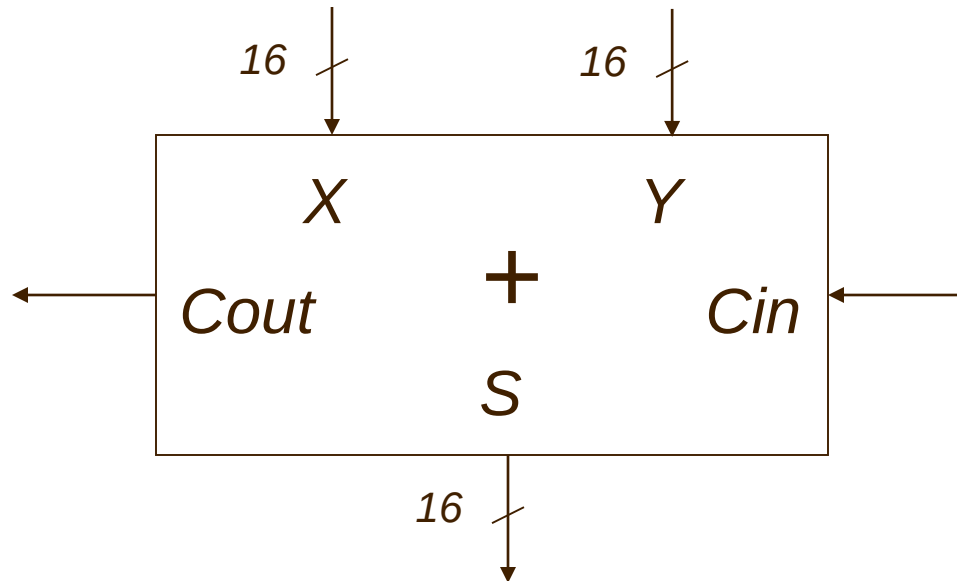

Addition of Unsigned Numbers (1)

```
LIBRARY ieee ;  
USE ieee.std_logic_1164.all ;  
USE ieee.numeric_std.all ;
```

```
ENTITY adder16 IS  
    PORT ( Cin          : IN      STD_LOGIC ;  
          X             : IN      STD_LOGIC_VECTOR(15 DOWNT0 0) ;  
          Y             : IN      STD_LOGIC_VECTOR(15 DOWNT0 0) ;  
          S             : OUT     STD_LOGIC_VECTOR(15 DOWNT0 0) ;  
          Cout          : OUT     STD_LOGIC ) ;  
END adder16 ;
```

Addition of Unsigned Numbers (3)

ARCHITECTURE dataflow OF adder16 IS

 signal USum: **unsigned(16 DOWNT0 0)** ;

 signal UCin: **unsigned(0 downto 0)**;

BEGIN

 UCin(0) <= Cin;

USum <= unsigned('0' & X) + unsigned(Y) + UCin;

 S <= std_logic_vector(USum(15 downto 0));

 Cout <= USum(16) ;

END dataflow ;

IEEE numeric_std package

- *How to infer arithmetic operators?*
- *In standard VHDL:*
signal a, b, sum: integer;
...
sum <= a + b;
- What's wrong with integer data type?

- *IEEE numeric_std package: define integer as an array of elements of std_logic*
- *Two new data types: unsigned, signed*
- *The array interpreted as an unsigned or signed binary number*
- *E.g.,*
***signal** x, y: signed(15 **downto** 0);*
- *Need invoke package to use the data type*
***library** ieee;*
***use** ieee.std_logic_1164.**all**;*
***use** ieee.numeric_std.**all**;*

Overloaded operators in *IEEE numeric_std* package

overloaded operator	description	data type of operand a	data type of operand b	data type of result
abs a - a	absolute value negation	signed		signed
a * b a / b a mod b a rem b a + b a - b	arithmetic operation	unsigned unsigned, natural signed signed, integer	unsigned, natural unsigned signed, integer signed	unsigned unsigned signed signed
a = b a /= b a < b a <= b a > b a >= b	relational operation	unsigned unsigned, natural signed signed, integer	unsigned, natural unsigned signed, integer signed	boolean boolean boolean boolean

- *E.g.*,

```
signal a, b, c, d: unsigned(7 downto 0);  
.  
.  
.  
a <= b + c;  
d <= b + 1;  
e <= (5 + a + b) - c;
```

Type conversion

- *Std_logic_vector, unsigned, signed are defined as an array of element of std_logic*
- *They considered as three different data types in VHDL*
- *Type conversion between data types:*
 - *type conversion function*
 - *Type casting (for “closely related” data types)*

Type conversion between number-related data types

data type of a	to data type	conversion function / type casting
unsigned, signed	std_logic_vector	std_logic_vector(a)
signed, std_logic_vector	unsigned	unsigned(a)
unsigned, signed	std_logic_vector	std_logic_vector(a)
unsigned, signed	integer	to_integer(a)
natural	unsigned	to_unsigned(a, size)
integer	signed	to_signed(a, size)

- *E.g.*

library ieee;

use ieee.std_logic_1164.all;

use ieee.numeric_std.all;

. . .

signal s1, s2, s3, s4, s5, s6: std_logic_vector(3 downto 0);

signal u1, u2, u3, u4, u6, u7: unsigned(3 downto 0);

signal sg: signed(3 downto 0);

– *Ok*

u3 <= u2 + u1; --- ok, both operands unsigned

u4 <= u2 + 1; --- ok, operands unsigned and natural

– *Wrong*

u5 <= sg; -- type mismatch

u6 <= 5; -- type mismatch

– *Fix*

u5 <= unsigned(sg); -- type casting

u6 <= to_unsigned(5,4); -- conversion function

– *Wrong*

u7 <= sg + u1; -- + undefined over the types

– *Fix*

u7 <= unsigned(sg) + u1; -- ok, but be careful

– *Wrong*

s3 <= u3; -- type mismatch

s4 <= 5; -- type mismatch

– *Fix*

s3 <= std_logic_vector(u3); -- type casting

s4 <= std_logic_vector(to_unsigned(5,4));

– *Wrong*

s5 <= s2 + s1; + undefined over std_logic_vector

s6 <= s2 + 1; + undefined

– *Fix*

s5 <= std_logic_vector(unsigned(s2) + unsigned(s1));

s6 <= std_logic_vector(unsigned(s2) + 1);

Multipliers



High Performance

CoolClock

Low Power

DataCache

Unsigned vs. Signed Multiplication


Unsigned

$$\begin{array}{r} 1111 \quad 15 \\ \times 1111 \quad \times 15 \\ \hline 11100001 \quad 225 \end{array}$$


Signed

$$\begin{array}{r} 1111 \quad -1 \\ \times 1111 \quad \times -1 \\ \hline 00000001 \quad 1 \end{array}$$


8x8-bit Unsigned Multiplier

 

8x8-bit Signed Multiplier

 

8x8-bit Unsigned and Signed Multiplier

 

Multiplication of signed and unsigned numbers

```
LIBRARY ieee;  
USE ieee.std_logic_1164.all;  
USE ieee.numeric_std.all ;
```

entity multiply is

port(

a : in STD_LOGIC_VECTOR(7 downto 0);

b : in STD_LOGIC_VECTOR(7 downto 0);

cu : out STD_LOGIC_VECTOR(15 downto 0);

cs : out STD_LOGIC_VECTOR(15 downto 0)

);

end multiply;

architecture dataflow of multiply is

begin

-- signed multiplication

cs <= STD_LOGIC_VECTOR(SIGNED(a)*SIGNED(b));

-- unsigned multiplication

cu <= STD_LOGIC_VECTOR(UNSIGNED(a)*UNSIGNED(b));

end dataflow;

High Performance


CoolClock

Low Power

DataCache



ROM 8x16 example (1)

 

ROM 8x16 example (2)

```
LIBRARY ieee;
USE ieee.std_logic_1164.all;
USE ieee.numeric_std.all;

ENTITY rom IS

    PORT (
        Addr : IN STD_LOGIC_VECTOR(2 DOWNTO 0);
        Dout : OUT STD_LOGIC_VECTOR(15 DOWNTO 0)
    );

END rom;
```

ROM 8x16 example (3)

ARCHITECTURE dataflow OF rom IS

SIGNAL temp: INTEGER RANGE 0 TO 7;

TYPE vector_array IS ARRAY (0 to 7) OF STD_LOGIC_VECTOR(15 DOWNT0 0);

CONSTANT memory : vector_array :=

```
(      X"800A",  
        X"D459",  
        X"A870",  
        X"7853",  
        X"650D",  
        X"642F",  
        X"F742",  
        X"F548");
```

BEGIN

temp <= to_integer(unsigned(Addr));

Dout <= memory(temp);

END dataflow;

ROM 8x16 example (4)

ARCHITECTURE dataflow OF rom IS

TYPE vector_array IS ARRAY (0 to 7) OF STD_LOGIC_VECTOR(15 DOWNT0 0);

CONSTANT memory : vector_array :=

```
(      X"800A",  
        X"D459",  
        X"A870",  
        X"7853",  
        X"650D",  
        X"642F",  
        X"F742",  
        X"F548");
```

BEGIN

Dout <= memory(to_integer(unsigned(Addr)));

END dataflow;

ECE 448

Lecture 4

Sequential-Circuit Building Blocks

Constants & Packages

Mixing Description Styles

Reading

Required

- P. Chu, *FPGA Prototyping by VHDL Examples*
Chapter 4, Regular Sequential Circuit

Recommended

- S. Brown and Z. Vranesic, *Fundamentals of Digital Logic with VHDL Design*
Chapter 7, Flip-Flops, Registers, Counters, and a Simple Processor



Counters

High Performance

CoolClock


Low Power

Detachable

2-bit up-counter with synchronous reset

```
LIBRARY ieee ;
USE ieee.std_logic_1164.all ;
USE ieee.numeric_std.all ;
ENTITY upcount IS
    PORT ( Clear, Clock      : IN          STD_LOGIC ;
          Q                  : OUT       STD_LOGIC_VECTOR(1 DOWNTO 0) );
END upcount ;
```

 
```
ARCHITECTURE behavioral OF upcount IS
    SIGNAL Count : unsigned(1 DOWNTO 0);
BEGIN
    upcount: PROCESS ( Clock )
    BEGIN
        IF rising_edge(Clock) THEN
            IF Clear = '1' THEN
                Count <= "00" ;
            ELSE
                Count <= Count + 1 ;
            END IF ;
        END IF;
    END PROCESS;
    Q <= std_logic_vector(Count);
END behavioral;
```



4-bit up-counter with asynchronous reset (1)

```
LIBRARY ieee ;  
USE ieee.std_logic_1164.all ;  
USE ieee.numeric_std.all ;
```
 
```
ENTITY upcount_ar IS  
    PORT ( Clock, Resetn, Enable : IN      STD_LOGIC ;  
          Q : OUT STD_LOGIC_VECTOR (3 DOWNTO 0)) ;  
END upcount_ar ;
```



4-bit up-counter with asynchronous reset (2)

ARCHITECTURE behavioral OF upcount_ar IS

SIGNAL Count : UNSIGNED (3 DOWNT0 0) ;

BEGIN

PROCESS (Clock, Resetn)

BEGIN

IF Resetn = '0' THEN

Count <= "0000" ;

ELSIF rising_edge(Clock) THEN

IF Enable = '1' THEN

Count <= Count + 1 ;


END IF ;

END IF ;

END PROCESS ;

Q <= std_logic_vector(Count) ;

END behavioral ;

 

Shift Registers




High Performance

CoolClock


Low Power

DataCache

Shift register – internal structure

 


Shift Register With Parallel Load

 

4-bit shift register with parallel load (1)

```
LIBRARY ieee ;
USE ieee.std_logic_1164.all ;

 ENTITY shift4 IS
    PORT ( D      : IN      STD_LOGIC_VECTOR(3 DOWNTO 0) ;
          Enable  : IN      STD_LOGIC ;
          Load    : IN      STD_LOGIC ;
          Sin      : IN      STD_LOGIC ;
          Clock    : IN      STD_LOGIC ;
          Q       : OUT     STD_LOGIC_VECTOR(3 DOWNTO 0) ) ;
END shift4 ;
```



4-bit shift register with parallel load (2)

ARCHITECTURE behavioral OF shift4 IS

SIGNAL Qt : STD_LOGIC_VECTOR(3 DOWNT0 0);

BEGIN

PROCESS (Clock)

BEGIN

IF rising_edge(Clock) THEN

IF Enable = '1' THEN

IF Load = '1' THEN

Qt <= D ;

ELSE

Qt <= Sin & Qt(3 downto 1);

END IF ;


END IF;

END IF ;

END PROCESS ;

Q <= Qt;

END behavioral ;

 

N -bit shift register with parallel load (1)

LIBRARY ieee ;

USE ieee.std_logic_1164.all ;

ENTITY shiftn IS

GENERIC (N : INTEGER := 8) ;

PORT (D : IN STD_LOGIC_VECTOR(**N-1** DOWNT0 0) ;

Enable : IN STD_LOGIC ;


Load : IN STD_LOGIC ;

Sin : IN STD_LOGIC ;

Clock : IN STD_LOGIC ;

Q : **OUT** STD_LOGIC_VECTOR(**N-1** DOWNT0 0)) ;

END shiftn ;

 

N-bit shift register with parallel load (2)

ARCHITECTURE behavioral OF shiftn IS

SIGNAL Qt: STD_LOGIC_VECTOR(N-1 DOWNT0 0);

BEGIN

PROCESS (Clock)

BEGIN

IF rising_edge(Clock) THEN

IF Enable = '1' THEN

IF Load = '1' THEN

Qt <= D ;

ELSE

Qt <= Sin & Qt(N-1 downto 1);

END IF ;


END IF;

END IF ;

END PROCESS ;

Q <= Qt;

END behavior al;

 

Sequential Logic Synthesis for Beginners



For Beginners


Use processes with very simple structure only to describe

- registers*
- shift registers*
- counters*
- state machines.*

Use examples discussed in class as a template.

*Create **generic** entities for registers, shift registers, and counters, and instantiate the corresponding components in a higher level circuit using GENERIC MAP PORT MAP.*

Supplement sequential components with combinational logic described using concurrent statements.

 The background is a light blue collage featuring various electronic components and text. At the top left, the words "High Performance" are written in a large, white, sans-serif font. At the top right, "CoolClock" is written in a similar font. In the center, a large, detailed image of a CPU chip is visible, with "CoolClock-II" printed on its surface. At the bottom left, the words "Low Power" are written in a large, white, sans-serif font. At the bottom right, "DataCache" is written in a similar font. Several circular and rectangular icons are scattered around the central text, including a server rack, a circuit board, a mobile phone, a keyboard, and a small electronic device.

Sequential Logic Synthesis for Intermediates

For Intermmmediates

1. *Use Processes with IF and CASE statements only. Do not use LOOPS or VARIABLES.*
2. *Sensitivity list of the PROCESS should include **only** signals that can by themsleves change the outputs of the sequential circuit (typically, clock and asynchronous set or reset)*
3. *Do not use PROCESSES without sensitivity list (they can be synthesizable, but make simulation inefficient)*

For Intermmmediates (2)

Given a single signal, the assignments to this signal should only be made within a single process block in order to avoid possible conflicts in assigning values to this signal.

~~Process 1: PROCESS (a, b)
BEGIN
 y <= a AND b;
END PROCESS;~~

~~Process 2: PROCESS (a, b)
BEGIN
 y <= a OR b;
END PROCESS;~~

Non-synthesizable VHDL

Delays

Delays are not synthesizable

Statements, such as

***wait for** 5 ns*

*a <= b **after** 10 ns*

*will not produce the required delay, and
should not be used in the code intended
for synthesis.*

Initializations

Declarations of signals (and variables) with initialized values, such as

SIGNAL a : STD_LOGIC := '0' ;

cannot be synthesized, and thus should be avoided.

If present, they will be ignored by the synthesis tools.

Use set and reset signals instead.

Dual-edge triggered register/counter (1)

In FPGAs register/counter can change only at either rising (default) or falling edge of the clock.

Dual-edge triggered clock is not synthesizable correctly, using either of the descriptions provided below.

Dual-edge triggered register/counter (2)

```
PROCESS (clk)
BEGIN
    IF (clk'EVENT AND clk='1' ) THEN
        counter <= counter + 1;
    ELSIF (clk'EVENT AND clk='0' ) THEN
        counter <= counter + 1;
    END IF;
END PROCESS;
```

Dual-edge triggered register/counter (3)

```
PROCESS (clk)
BEGIN
    IF (clk'EVENT) THEN
        counter <= counter + 1;
    END IF;
END PROCESS;
```

```
PROCESS (clk)
BEGIN
    counter <= counter + 1;
END PROCESS;
```