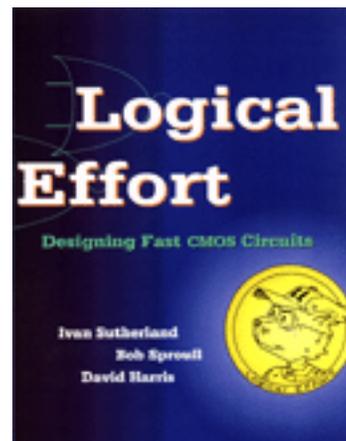


Logical Effort

Sizing Transistors for Speed

Estimating Delays

- ◆ Would be nice to have a “back of the envelope” method for sizing gates for speed
- ◆ Logical Effort
 - Book by Sutherland, Sproull, Harris
 - Chapter 1 is on our web page
 - Also Chapter 4 in our textbook



Gate Delay Model

- ◆ First, normalize a model of delay to dimensionless units to isolate fabrication effects
- ◆ $d_{\text{abs}} = d \tau$
 - τ is the delay of a minimum inverter driving another minimum inverter with no parasitics
 - In a 0.6 μ process, this is approx 40ps
 - Now we can think about delay in terms of d and scale it to whatever process we're using

Gate Delay


- ◆ Delay of a gate d has two components
 - A fixed part called *parasitic delay* p
 - A part proportional to the load on the output called the *effort delay* or *stage effort* f
 - *Total delay* is measured in units of τ , and is sum of these delays
- ◆ $d = f + p$

Effort Delay

- ◆ The **effort delay** (due to load) can be further broken down into two terms: $f = g * h$
 - g = **logical effort** which captures properties of the gate's structure
 - h = **electrical effort** which captures properties of load and transistor sizes
 - $h = C_{out}/C_{in}$
 - C_{out} is capacitance that loads the output
 - C_{in} is capacitance presented at the input
 - So, $d = gh + p$


Logical Effort

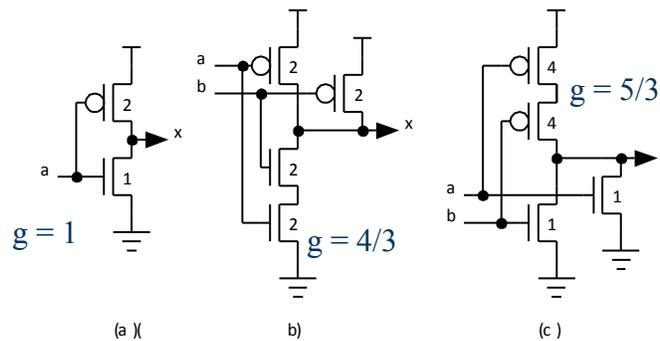- ◆ Logical effort normalizes the output drive capability of a gate to match a unit inverter
 - How much **more** input capacitance does a gate need to present to offer the **same** drive as an inverter?




Computing Logical Effort

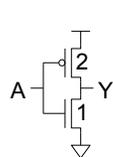- DEF: *Logical effort is the ratio of the input capacitance of a gate to the input capacitance of an inverter delivering the same output current.*
- Measure from delay vs. fanout plots
- Or estimate by counting transistor widths




$$C_{in} = 3$$

$$g = 3/3$$

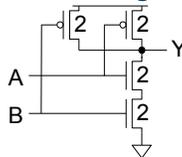

$$C_{in} = 4$$

$$g = 4/3$$

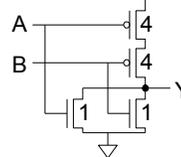

$$C_{in} = 5$$

$$g = 5/3$$

Logical Effort of Other Gates

- Logical effort of common gates assuming that P/N size ratio is 2

Number of inputs

Gate Type	1	2	3	4	5	n
Inverter	1					
NAND		4/3	5/3	6/3	7/3	$(n+2)/3$
NOR		5/3	7/3	9/3	11/3	$(2n+1)/3$
MUX		2	2	2	2	2
XOR		4	12	32		


Electrical Effort

- ◆ Value of **logical effort** g is independent of transistor size
 - It's related to the ratios and the topology
- ◆ **Electrical effort** h captures the drive capability of the transistors via sizing
 - Electrical effort $h = C_{out}/C_{in}$
 - Note that as transistor sizes for a gate increase, h decreases because C_{in} goes up


Parasitic Delay

- ◆ Parasitic delay p is caused by the internal capacitance of the gate
 - It's constant and independent of transistor size
 - As you increase the transistor size, you also increase the cap of the gate/source/drain areas which keeps it constant
 - For our purposes, normalize p_{inv} to 1
 - N-input NAND = $n * p_{inv}$
 - N-input NOR = $n * p_{inv}$
 - N-way mux = $2n * p_{inv}$
 - XOR = $4 * p_{inv}$

Plots of Gate Delay

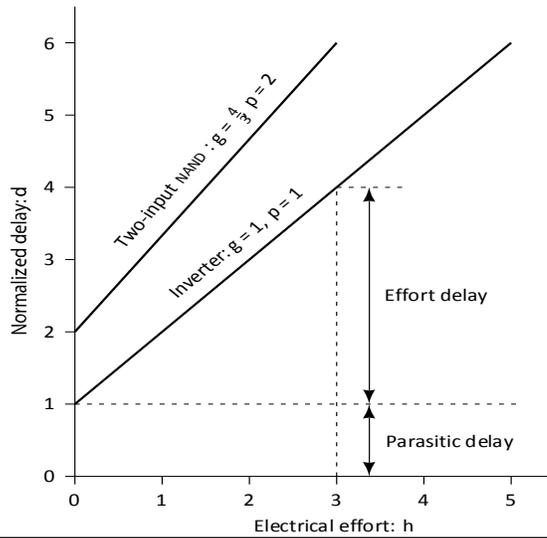

Delay Estimation

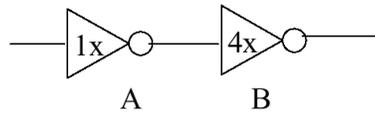


Remember, τ in
Our process $\sim 40\text{ps}$

$$A_delay = g \cdot h + p = 1 \cdot (C_{inB}/C_{inA}) + 1$$

$$= 1 \cdot (4 \cdot C_{inA}/C_{inA}) + 1 = 4 + 1 = 5 \text{ time units}$$

$\sim 200\text{ps}$

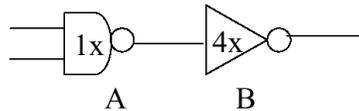

$$A_delay = g \cdot h + p = (4/3) \cdot (C_{inB}/C_{inA}) + 2 \cdot 1$$


$$C_{in_B} = 4 \cdot 3 = 12, \quad C_{in_A} = 4$$

$$A_delay = (4/3) \cdot (12/4) + 2 = 4 + 2 = 6 \text{ units} \quad \sim 240\text{ps}$$

Nand2 worse because of higher parasitic delay than inverter.


Note that $g \cdot h$ term was same for both because NAND2 sized to provide same current drive.

Delay Estimation

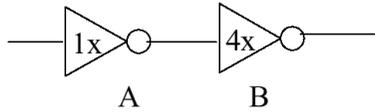

Remember, τ in
Our process $\sim 40\text{ps}$
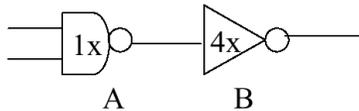
$$\begin{aligned} A_delay &= g \cdot h + p = 1 \cdot (\text{Cin}_B / \text{Cin}_A) + 1 && \sim 200\text{ps} \\ &= 1 \cdot (4 \cdot \text{Cin}_A / \text{Cin}_A) + 1 = 4 + 1 = 5 \text{ time units} \end{aligned}$$



τ in 180nm $\sim 12\text{ps}$
FO4 Inverter delay = 60ps
FO4 NAND delay = 72ps


$$\begin{aligned} A_delay &= g \cdot h + p = (4/3) \cdot (\text{Cin}_B / \text{Cin}_A) + 2 \cdot 1 \\ \text{Cin}_B &= 4 \cdot 3 = 12, \quad \text{Cin}_A = 4 \\ A_delay &= (4/3) \cdot (12/4) + 2 = 4 + 2 = 6 \text{ units} && \sim 240\text{ps} \end{aligned}$$

Nand2 worse because of higher parasitic delay than inverter.

Note that $g \cdot h$ term was same for both because NAND2 sized to provide same current drive.

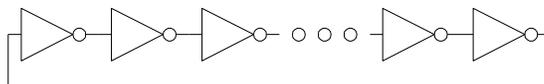Example: Ring Oscillator

- Estimate the frequency of an N-stage ring oscillator



Logical Effort: $g =$

Electrical Effort: $h =$


Parasitic Delay: $p =$

Stage Delay: $d =$

Period of osc =

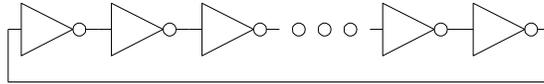Example: Ring Oscillator

- Estimate the frequency of an N-stage ring oscillator



Logical Effort: $g = 1$

Electrical Effort: $h = 1$

Parasitic Delay: $p = 1$


Stage Delay: $d = 2$ so $d_{\text{abs}} = 80\text{ps}$

Period: $2 \cdot N \cdot d_{\text{abs}} = 4.96\text{ns}$, Freq = $\sim 200\text{MHz}$

For $N = 31$

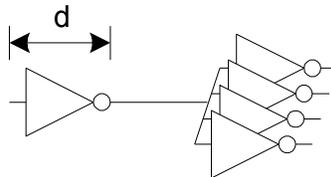Example: FO4 Inverter

- Estimate the delay of a fanout-of-4 (FO4) inverter



Logical Effort: $g =$


Electrical Effort: $h =$

Parasitic Delay: $p =$

Stage Delay: $d =$

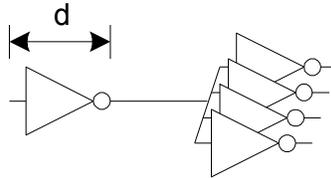Example: FO4 Inverter


- Estimate the delay of a fanout-of-4 (FO4) inverter



The FO4 delay is about
 200 ps in 0.6 μm process
 60 ps in a 180 nm process
 $f/3$ ns in an f μm process

Logical Effort: $g = 1$
 Electrical Effort: $h = 4$
 Parasitic Delay: $p = 1$
 Stage Delay: $d = gh + p = 5$

Delay Estimation

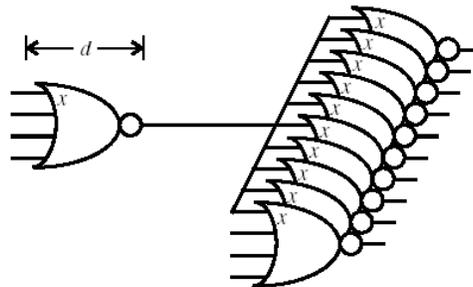


- If $C_{in} = x$, $C_{out} = 10x$, thus $h = 10$
- $g = 9/3 = 3$
- $d = gh + p = 3 \cdot 10 + 4 \cdot 1 = 34$ (1360 ps)

Multi Stage Delay

MultiStage Delay

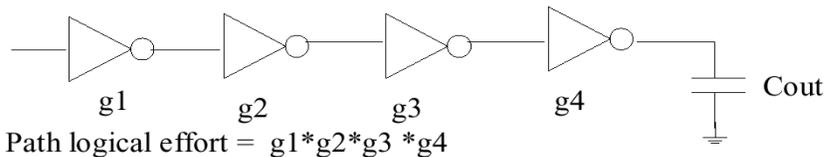- Recall rule of thumb that said to balance the delay at each stage along a critical path
- Concepts of logical effort and electrical effort can be generalized to multistage paths




In general, Path logic effort $G = \prod g(i)$

Path electrical effort $H = C_{out} / C_{in_first_gate}$

Must remember that electrical effort only is concerned with effect of logic network on input drivers and output load.

Off-Path Load

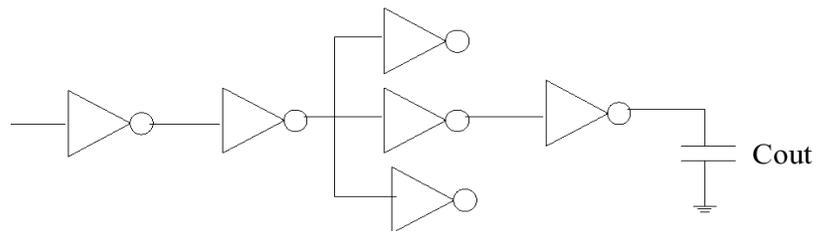

Off path load will divert electrical effort from the main path, must account for this. Define a *branching effort* b as:

$$b = (C_{con_path} + C_{off_path}) / C_{con_path} \quad \frac{C_{total}}{C_{useful}}$$

The branching effort will modify the electrical effort needed at that stage. The branch effort B of the path is:

$$B = \prod b(i)$$

Summary – multistage networks

- ◆ Logical effort generalizes to multistage networks

- ◆ *Path Logical Effort* $G = \prod g_i$

- ◆ *Path Electrical Effort* $H = \frac{C_{out-path}}{C_{in-path}}$

- ◆ *Path Effort* $F = \prod f_i = \prod g_i h_i$

- ◆ Can we write $F = GH$?

Branching Effort

- ◆ Remember *branching effort*
 - Accounts for branching between stages in path

$$b = \frac{C_{on\ path} + C_{off\ path}}{C_{on\ path}}$$
$$B = \prod b_i$$

Note:
 $\prod h_i = BH$

- ◆ Now we compute the path effort
 - $F = GBH$

Multistage Delays

- ◆ Path Effort Delay $D_F = \sum f_i$
- ◆ Path Parasitic Delay $P = \sum p_i$
- ◆ Path Delay $D = \sum d_i = D_F + P$

Designing Fast Circuits

$$D = \sum d_i = D_F + P$$

- ◆ Delay is smallest when each stage bears same effort
$$\hat{f} = g_i h_i = F^{\frac{1}{N}}$$
- ◆ Thus the minimum delay of N stage path is
$$D = NF^{\frac{1}{N}} + P$$
- ◆ This is a **key** result of logical effort
 - Find fastest possible delay
 - Doesn't require calculating gate sizes

Minimizing Path Delay

The absolute delay will have the parasitic delays of each stage summed together.

However, can *focus on just Path effort F* for minimization purposes since parasitic delays are constant.

For an N-stage network, *the path delay is least when each stage in the path bears the same stage effort.*

$$f(\min) = g(i) * h(i) = F^{1/N}$$

Minimum achievable path delay

$$D(\min) = N * F^{1/N} + P$$

Note that if N=1, then $d = f + p$, the original single gate equation.

Choosing Transistor Sizes

Remember that the stage effort $h(i)$ is related to transistor sizes.

$$f(\min) = g(i) * h(i) = F^{1/N}$$


So

$$h(i) \min = F^{1/N} / g(i)$$

To size transistors, start at end of path, and compute:

$$C_{in}(i) = g_i * C_{out}(i) / f(\min)$$

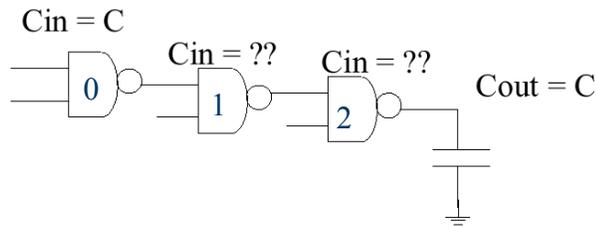Once $C_{in}(i)$ is known, can distribute this among transistors of that stage.



Size the transistors of the nand2 gates for the three stages shown.

$$\text{Path logic effort} = G = g_0 * g_1 * g_2 = 4/3 * 4/3 * 4/3 = 2.37$$

$$\text{Branching effort } B = 1.0 \text{ (no off-path load)}$$

$$\text{Electrical effort } H = \text{Cout}/\text{Cin} = C/C = 1.0$$

$$\begin{aligned} \text{Min delay achievable} &= 3 * (G * B * H)^{1/3} + 3 * (2 * \text{pinv}) \\ &= 3 * (2.37 * 1 * 1)^{1/3} + 3 * (2 * 1.0) = 10.0 \\ \text{minD} &= N * F^{1/N} + P = 3 * (1.3333) + 6 = 10 \end{aligned}$$

Example, continued

The effort of each stage will be:

$$f_{\min} = (G * B * H)^{1/3} = (2.37 * 1.0 * 1.0)^{1/3} = 1.33 = 4/3$$

Cin of last gate should equal: $f(\min) = g_i * b_i * h_i$


$$\begin{aligned} \text{Cin last gate (min)} &= g_i * \text{Cout (i)} / f(\min) \\ &= 4/3 * C / (4/3) = C \end{aligned}$$

Cin of middle gate should equal:

$$\begin{aligned} \text{Cin middle gate} &= g_i * \text{Cin last gate} / f(\min) \\ &= 4/3 * C / (4/3) = C \end{aligned}$$

All gates have same input capacitance, distribute it among transistors.

Transistor Sizes for Example

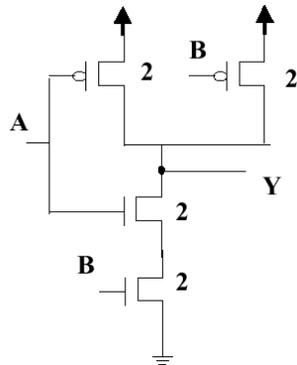


Where gate capacitance of
 $2 * W * L$ Mosfet = $C/2$

Choose W accordingly.

Another Example, Larger Load

Let Load = $8C$, what changes?

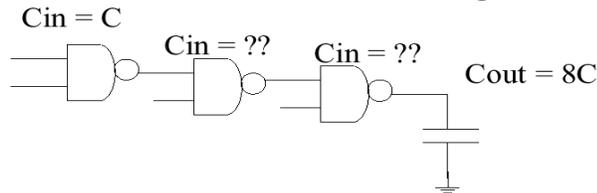

Size the transistors of the nand2 gates for the three stages shown.

$$\text{Path logic effort} = G = g_0 * g_1 * g_2 = 4/3 * 4/3 * 4/3 = 2.37$$

Branching effort $B = 1.0$ (no off-path load)

$$\text{Electrical effort } H = C_{out}/C_{in} = 8C/C = 8.0$$

$$\begin{aligned} \text{Min delay achievable} &= 3 * (G * B * H)^{1/3} + 3 * (2 * p_{inv}) \\ &= 3 * (2.37 * 1 * 8)^{1/3} + 3 * (2 * 1.0) = 14.0 \end{aligned}$$

8C Load Example Cont.

The effort of each stage will be:

$$f_{\min} = (G \cdot B \cdot H)^{1/3} = (2.37 \cdot 1.0 \cdot 8)^{1/3} = 2.67 = 8/3$$

Cin of last gate should equal:


$$\begin{aligned} C_{\text{in last gate (min)}} &= g_i \cdot C_{\text{out (i)}} / f(\min) \\ &= 4/3 \cdot 8C / (8/3) = 4C \end{aligned}$$

Cin of middle gate should equal:

$$\begin{aligned} C_{\text{in middle gate}} &= g_i \cdot C_{\text{in last gate}} / f(\min) \\ &= 4/3 \cdot 4C / (8/3) = 2C \end{aligned}$$

Note that each stage gets progressively larger, as is typical with a multi-stage path driving a large load.

Example 1.6 from Chap 1

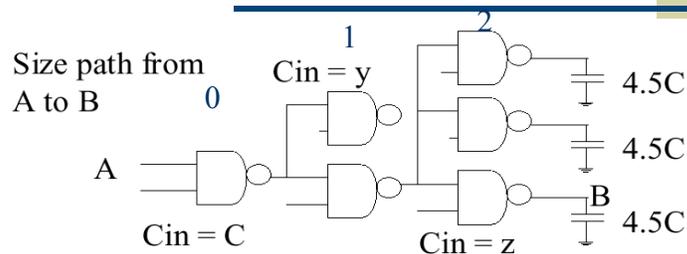

$$\text{Path logic effort } G = g_0 \cdot g_1 \cdot g_2 = 4/3 \cdot 4/3 \cdot 4/3 = 2.37$$

$$\text{Branch effort, 1st stage} = (y+y)/y = 2.$$

$$\text{Branch effort, 2nd stage} = (z+z+z)/z = 3$$

$$\text{Path Branch effort } B = 2 \cdot 3 = 6.$$

$$\text{Path electrical effort } H = C_{\text{out}}/C_{\text{in}} = 4.5C/C = 4.5$$

$$\text{Path stage effort} = F = G \cdot B \cdot H = 2.37 \cdot 6 \cdot 4.5 = 64.$$

$$\text{Min delay} = N(F)^{1/N} + P = 3 \cdot (64)^{1/3} + 3(2\text{pinv}) = 18.0 \text{ units}$$

Example 1.6 Continued

Stage effort of each stage should be:

$$f(\min) = (F)^{1/N} = (GBH)^{1/N} = (64)^{1/3} = 4$$

Determine C_{in} of last stage:

$$f(\min) = g_i * b_i * h_i$$

$$C_{in}(z) = g * C_{out} / f(\min) = 4/3 * 4.5C / 4 = 1.5 C$$

Determine C_{in} of middle stage:

$$C_{in}(y) = g * (3 * C_{in}(z)) / f(\min) = 4/3 * (3 * 1.5C) / 4 = 1.5C$$


Is first stage correct?

$$C_{in}(A) = g * (2 * C_{in}(y)) / f(\min) = 4/3 * (2 * 1.5C) / 4 = C.$$


Yes, self-consistent.

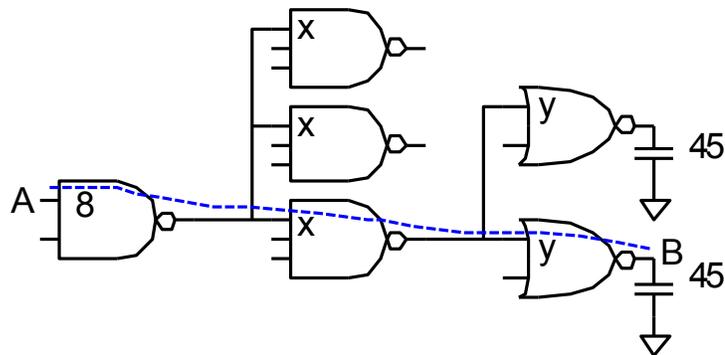Example: 3-stage path

- ◆ Select gate sizes x and y for least delay from A to B




Example: 3-stage path

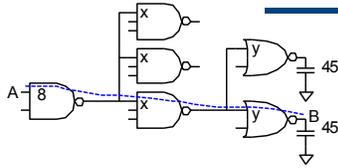

Logical Effort	$G =$
Electrical Effort	$H =$
Branching Effort	$B =$
Path Effort	$F =$
Best Stage Effort	$\hat{f} =$
Parasitic Delay	$P =$
Delay	$D =$

Example: 3-stage path

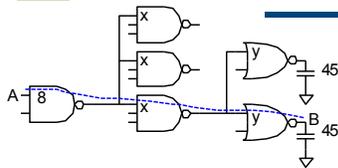


Logical Effort	$G = (4/3) * (5/3) * (5/3) = 100/27$
Electrical Effort	$H = 45/8$
Branching Effort	$B = 3 * 2 = 6$
Path Effort	$F = GBH = 125$
Best Stage Effort	$\hat{f} = \sqrt[3]{F} = 5$
Parasitic Delay	$P = 2 + 3 + 2 = 7$
Delay	$D = 3 * 5 + 7 = 22 = 4.4 \text{ FO4}$

Example: 3-stage path

- Work backward for sizes

y =

x =

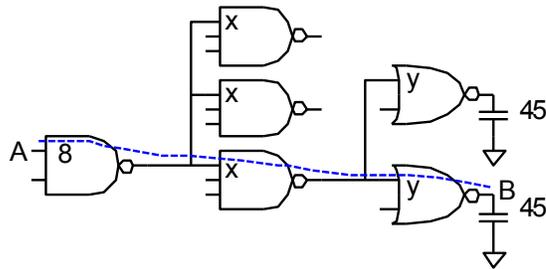



Example: 3-stage path

- Work backward for sizes $f(\min) = g_i * b_i * h_i$

$$y = 45 * (5/3) / 5 = 15 \quad (g_i * b_i * C_{out}) / f_{min} = C_{in}$$

$$x = (15 * 2) * (5/3) / 5 = 10$$

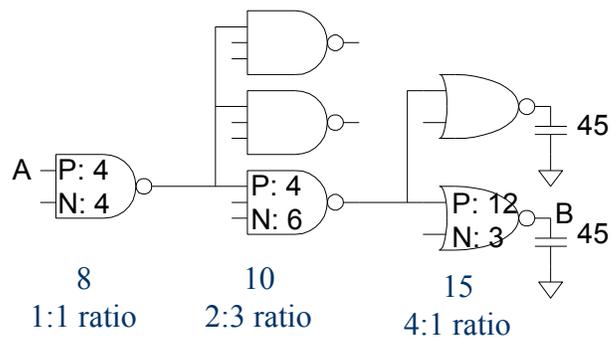

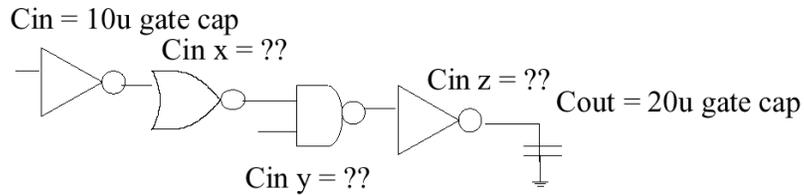

Path logic effort $G = g_0 * g_1 * g_2 * g_3 = 1 * 5/3 * 4/3 * 1 = 20/9$

Path Branch effort $B = 1$

Path electrical effort $H = C_{out}/C_{in} = 20/10 = 2$

Path stage effort = $F = G * B * H = (20/9) * 1 * 2 = 40/9$

For Min delay, each stage has effort $(F)^{1/N} = (40/9)^{1/4} = 1.45$

$z = g * C_{out}/f(\min) = 1 * 20 / 1.45 = 14$ $(g_i * b_i * C_{out}) / f_{\min} = C_{in}$

$y = g * C_{in}(z) / f(\min) = 4/3 * 14 / 1.45 = 13$

$x = g * C_{in}(y) / f(\min) = 5/3 * 13 / 1.45 = 15$


Note: Don't care about parasitics for gate sizing, only if you want to know absolute delay...

Misc. Comments

- ◆ Note that you never size the first gate
 - This gate is assumed to be fixed
 - If you were allowed to size it, the algorithm would try to make it as large as possible
- ◆ This is an estimation algorithm
 - Authors claim that sizing a gate by 1.5x too big or small still results in a path delay within 15% of minimum




Sensitivity Analysis

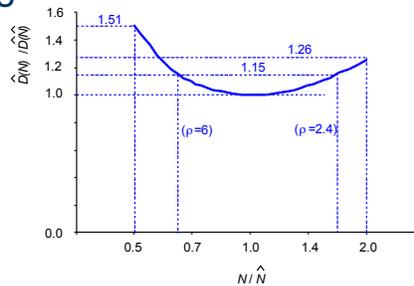- How sensitive is delay to using exactly the best number of stages?




- $2.4 < \rho < 6$ gives delay within 15% of optimal
 - We can be sloppy!
 - I like $\rho = 4$

Evaluating Different Options

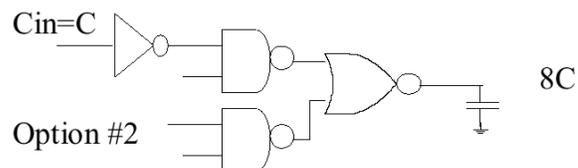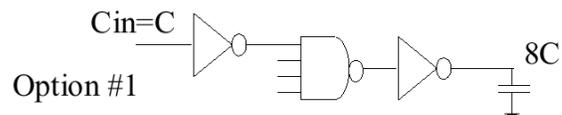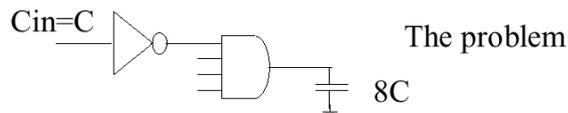

Option #1

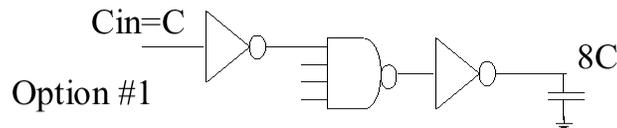

$$\text{Path logic effort } G = g_0 * g_1 * g_2 = 1 * 6/3 * 1 = 2$$


$$\text{Path Branch effort } B = 1$$

$$\text{Path electrical effort } H = C_{out}/C_{in} = 8C/C = 8$$

$$\text{Path stage effort } = F = G * B * H = 2 * 1 * 8 = 16$$

$$\begin{aligned} \text{Min delay: } &= N * (F)^{1/N} + P \\ &= 3 * (16)^{1/3} + (\text{pinv} + 4 * \text{pinv} + \text{pinv}) \\ &= 3 * (2.5) + 6 = \boxed{13.5} \end{aligned}$$

Option #2

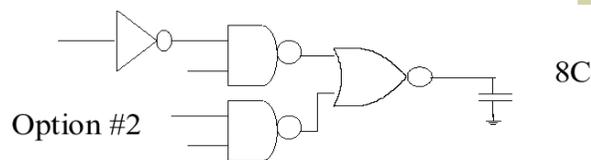

$$\text{Path logic effort } G = g_0 * g_1 * g_2 = 1 * 4/3 * 5/3 = 20/9$$

$$\text{Path Branch effort } B = 1$$

$$\text{Path electrical effort } H = C_{out}/C_{in} = 8C/C = 8$$

$$\text{Path stage effort } = F = G * B * H = 20/9 * 1 * 8 = 160/9$$

$$\begin{aligned} \text{Min delay: } &= N * (F)^{1/N} + P \\ &= 3 * (160/9)^{1/3} + (\text{pinv} + 2 * \text{pinv} + 2 * \text{pinv}) \\ &= 3 * 2.6 + 5 = \boxed{12.8} \end{aligned}$$

Option #2 appears to be better than Option #1, by a slight margin.

What if we consider gate area and power?
What about a 4-input NOR?

How many stages?

- ◆ Consider three alternatives for driving a load 25 times the input capacitance
 - One inverter
 - Three inverters in series
 - Five inverters in series
- ◆ They all do the job, but which one is fastest?

How many stages?

- ◆ In all cases: $G = 1$, $B = 1$, and $H = 25$
- ◆ Path delay is $N(25)^{1/N} + N P_{inv}$
 - $N = 1$, $D = 26$ units
 - $N = 3$, $D = 11.8$ units
 - $N = 5$, $D = 14.5$ units
- ◆ Since $N=3$ is best, each stage will bear an effort of $(25)^{1/3} = 2.9$
 - So, each stage is $\sim 3x$ larger than the last
 - In general, the best stage effort is between 3 and 4 (not e as often stated)
 - The e value doesn't use parasitics...

Choosing the Best # of Stages

- ◆ You can solve the delay equations to determine the number of stages N that will achieve the minimum delay
 - Approximate by $\text{Log}_4 F$

Path Effort F	Best N	Min Delay D	Stage effort f
0-5.83	1	1.0-6.8	0-5.8
5.83-22.3	2	6.8-11.4	2.4-4.7
22.3-82.2	3	11.4-16.0	2.8-4.4
82.2-300	4	16.0-20.7	3.0-4.2
300-1090	5	20.7-25.3	3.1-4.1
1090-3920	6	25.3-29.8	3.2-4.0

Example

- ◆ String of inverters driving an off-chip load
 - Pad cap and load = 40pf
 - Equivalent to 20,000 microns of gate cap
 - Assume first inverter in chain has 7.2u of input cap
 - How many stages in inv chain?
- ◆ $H = 20,000/7.2 = 2777$
- ◆ From the table, 6 stages is best
- ◆ Stage effort = $f = (2777)^{1/6} = 3.75$
- ◆ Path delay $D = 6*3.75 + 6*P_{\text{inv}} = 28.5$
 - $D = 1.14\text{ns}$ if $\tau = 40\text{ps}$

Other N's?

- ◆ $N=2: f=(2777)^{1/2} = 52.7$
 - $\text{delay} = 2(52.7) + 2 = 158.1 = 6.324\text{ns}$
- ◆ $N=3: f=(2777)^{1/3} = 14$
 - $\text{delay} = 3(14) + 3 = 45 = 1.8\text{ns}$
- ◆ $N=4: f=(2777)^{1/4} = 7.26$
 - $\text{delay} = 4(7.26) + 4 = 33.04 = 1.32\text{ns}$
- ◆ $N=5: f=(2777)^{1/5} = 4.88$
 - $\text{delay} = 5(4.88) + 5 = 29.4 = 1.18\text{ns}$
- ◆ $N=6: \text{delay} = 1.14\text{ns}$
- ◆ $N=7: f=(2777)^{1/7} = 3.105$
 - $\text{delay} = 7(3.105) + 7 = 28.7 = 1.15\text{ns}$

Summary

- ◆ Compute path effort $F = GBH$
- ◆ Use table, or estimate $N = \log_4 F$ to decide on number of stages
- ◆ Estimate minimum possible delay
$$D = NF^{1/N} + \sum p_i$$
- ◆ Add or remove stages in your logic to get close to N
- ◆ Compute effort at each stage $f_{\min} = F^{1/N}$
- ◆ Starting at output, work backwards to compute transistor sizes $C_{\text{in}} = (g_i * b_i * C_{\text{out}})/f_{\min}$

Limits of Logical Effort

- ◆ Chicken and egg problem
 - Need path to compute G
 - But don't know number of stages without G
- ◆ Simplistic delay model
 - Neglects input rise time effects
- ◆ Interconnect
 - Iteration required in designs with wire
- ◆ Maximum speed only
 - Not minimum area/power for constrained delay

Summary

- ◆ Logical effort is useful for thinking of delay in circuits
 - Numeric logical effort characterizes gates
 - NANDs are faster than NORs in CMOS
 - Paths are fastest when effort delays are ~ 4
 - Path delay is weakly sensitive to stages, sizes
 - But using fewer stages doesn't mean faster paths
 - Delay of path is about $\log_4 F$ FO4 inverter delays
 - Inverters and NAND2 best for driving large caps
- ◆ Provides language for discussing fast circuits
 - But requires practice to master