

Register Transfer Level

- Something between the logic level and the architecture level
- A convenient way to describe synchronous sequential systems
- State diagrams for pros

Hierarchy of Designs

- The design of a digital system happens in many different levels of abstraction
 - Physical level
 - Electronic level
 - Logic level
 - Architectural level
 - System level

Theory-Practice

- In theory, theory and practice are the same.
- In practice they are not
- Real systems tend to have many states with many transitions that depend on many inputs
- Simple state diagrams are not enough; we need a more powerful language

Modularity

- Using better notation is not enough
- We have to use another design concept called modularity
- We partition our design into many modules each one with its own specifications

Advantages

- Division of labor among members of the team
- Reuse the design of the modules in other systems
- Keep the size manageable.

They are not unrelated

- Modules and hierarchies of abstraction are not unrelated
- They both try to hide unnecessary information.

What we do here

- Design simple modules
- Implement our designs in the logic level
- Explore various possibilities

Components

- Registers (collections of F-F)
- Operations on registers (using combinational circuits)
- Control (someone to boss everything around)

Registers

- Registers are collections of F-F that can execute LOAD and other operations
- Sometimes the other operations are incrementing, decrementing, shifting, etc
- Sometimes these operations are done with the help of separate combinational circuits

For Example

- A 16-bit incrementer requires 16 half adders
 - more hardware if we seek efficiency
- If we need two counters that do not increment at the same time we might decide to let them share the incrementer.

Transfers

- This is done by transferring the data to the incrementer
- and then transferring the output of the incrementer back to the register

Transfer Notation

- We use statements like
 - $R1 \Leftarrow R2$
- e.g. R2 is copied into R1
- The transfer may be conditional
 - if (T1=1) then ($R1 \Leftarrow R2$)

Anything Goes

- $R1 \leq R2 + R3$
- $R3 \leq R3 + 1$
- $R4 \leq \text{shl } R4$
- $R5 \leq 0$
- The similarity with Verilog is obvious...

Like Verilog

- We want to describe
 - Transfer operations
 - Arithmetic operations
 - Logic operations
 - Shift operations

Clocked Transfer

- The transfer happens only at the edge of the clock
- Before the clock the combinational circuits are computing the input to the F-F
- After the clock we are computing the F-F input for the next state.

All Transfers at Once

- Since all transfers happen at once
- The natural procedural assignment is the non-blocking one:
 - $R1 \leq R2$
 - $R2 \leq R1$

Loops

- There are two uses of the loops:
 - describe test benches
 - describe repeated hardware

Example: for loop

```
module decoder (IN, Y);
  input [1:0] IN; //Two binary inputs
  output [3:0] Y; //Four binary outputs
  reg [3:0] Y;
  integer I; //control variable for loop
  always @ (IN)
    for (I = 0; I <= 3; I = I + 1)
      if (IN == I) Y[I] = 1;
      else Y[I] = 0;
endmodule
```

The Equivalent

- The **for** loop can be replaced by
 - if (N=00) F[0]=1; else F[0]=0;
 - if (N=01) F[1]=1; else F[1]=0;
 - if (N=10) F[2]=1; else F[2]=0;
 - if (N=11) F[3]=1; else F[3]=0;

Synthesis

- The hardware compiler should know how to do:
 - $B = A + C$ // addition
 - **assign** $Y = S ? I1 : I0$ // 2-1 MUX
 - **case** ... // larger MUX
 - **always** @ (**posedge** ...) // edge triggered F-F

The Design Process

- Like any design process, we have two phases
 - Compose
 - Verify
- Composition is (nowadays) done in a HDL
- Verification is done (mostly) with simulations

Various Simulations

- A simulation is just an approximation of the reality
- There are several kinds of approximations
 - RTL simulations
 - Gate level simulations
 - Electronic level simulations

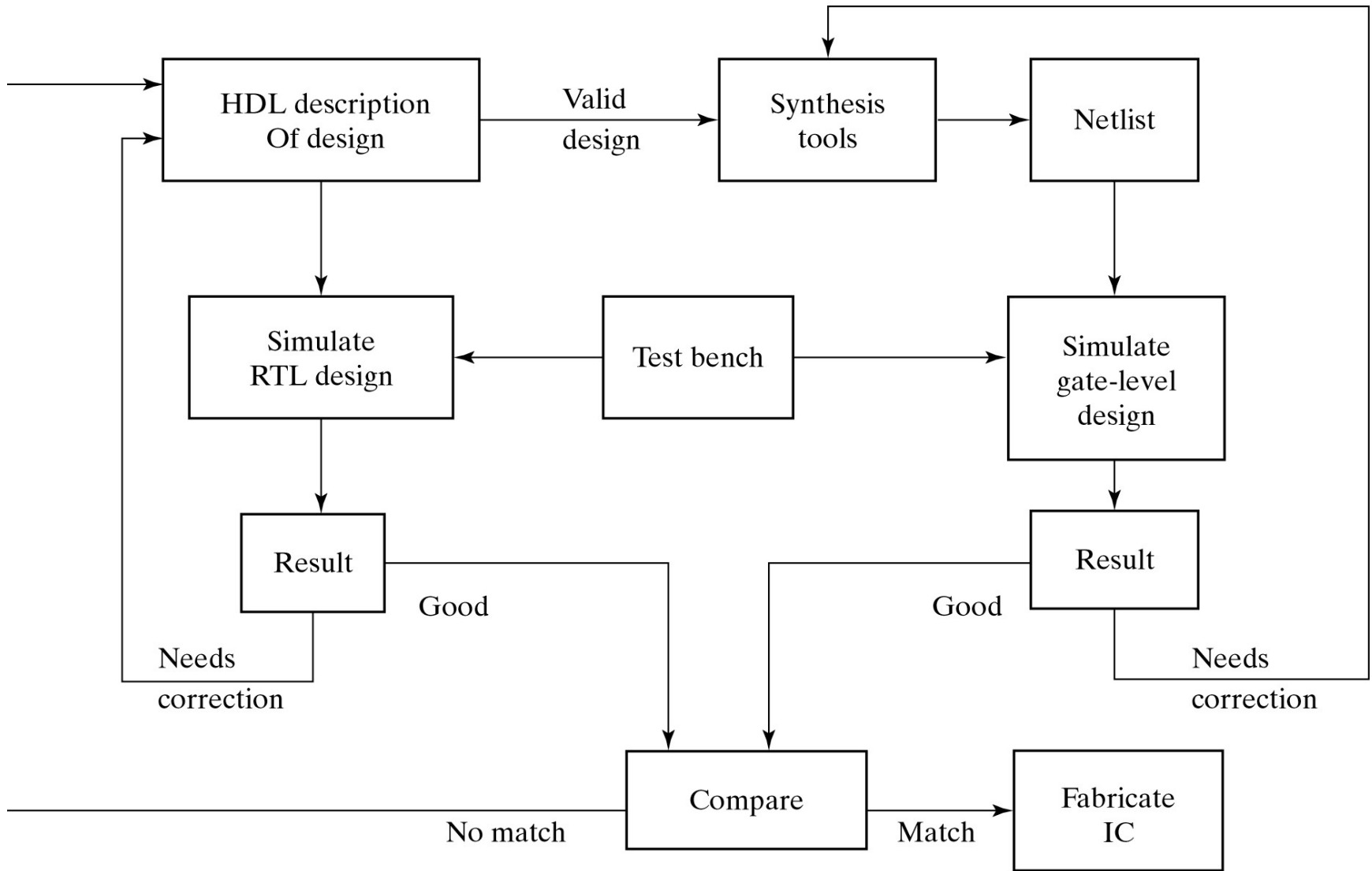


Fig. 8-1 Process of HDL Simulation and Synthesis

Algorithmic State Machines

- Synchronous sequential circuits can be thought of as having two parts
 - The *data* part that is concerned with the processing of the contents of the registers
 - The *control* part that is concerned with the sequencing of states

The Datapath

- Contains all the registers
- All the arithmetic etc logic that operates on the data
- All the outputs (to the world and to the logic unit)
- Receives commands from the control unit

Control Unit

- Contains all the “state” F-F
- All the logic to decide the next state
- Receives feedback from the data path
- Generates commands for things to happen in the datapath or just outputs its state

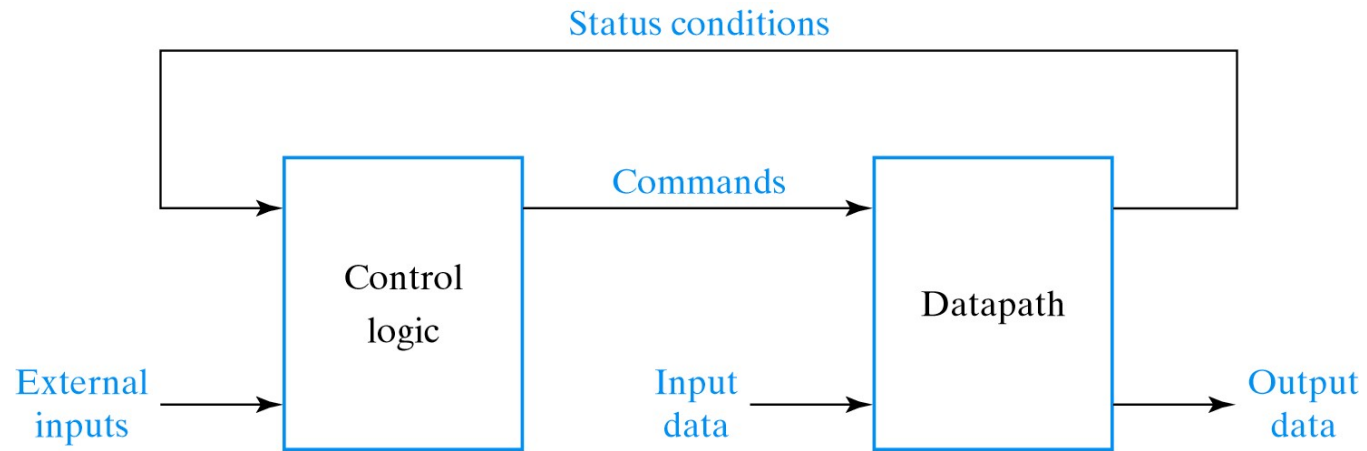


Fig. 8-2 Control and Datapath Interaction

ASM

- Part of the work to be done is to
 - Define a set of states
 - The operations that take place in every state
 - And the transitions between the states
- All this in a way that they solve a problem
- This is called an ASM

ASM Charts

- An ASM can be described with a HDL
- Can also be described with a kind of flowchart
 - Similar to s/w flowcharts, but adapted to hardware

State Box

- Represents a state (of course!)
- Contains
 - The symbolic state name
 - The binary state name (if available)
 - Any number of unconditional operations

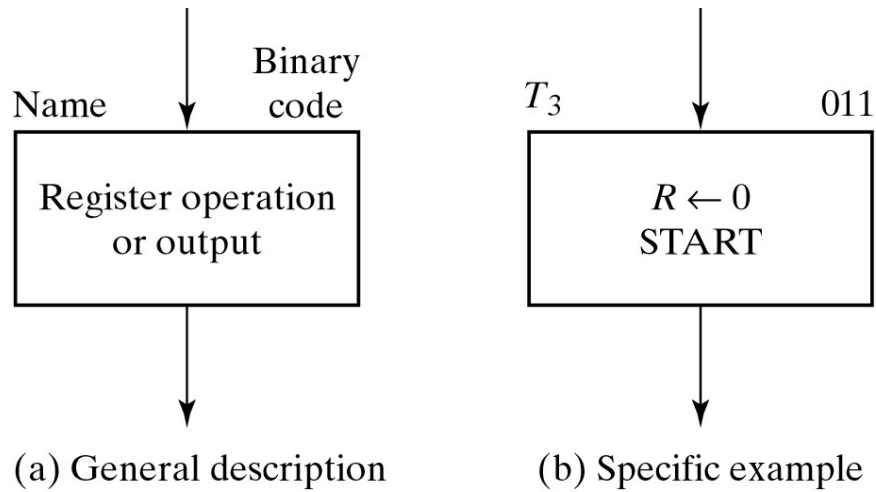


Fig. 8-3 State Box

Decision Box

- Represents a decision (of course!)
- Normally a binary decision
- Has one incoming arrow and two outgoing
- The condition is written inside
- The outcome on the outgoing arrows

 


Fig. 8-4 Decision Box

Conditional Box

- Represents a conditional statement (of course!)
- Always follows a decision box
- Contains the operations that will be executed if we reach it

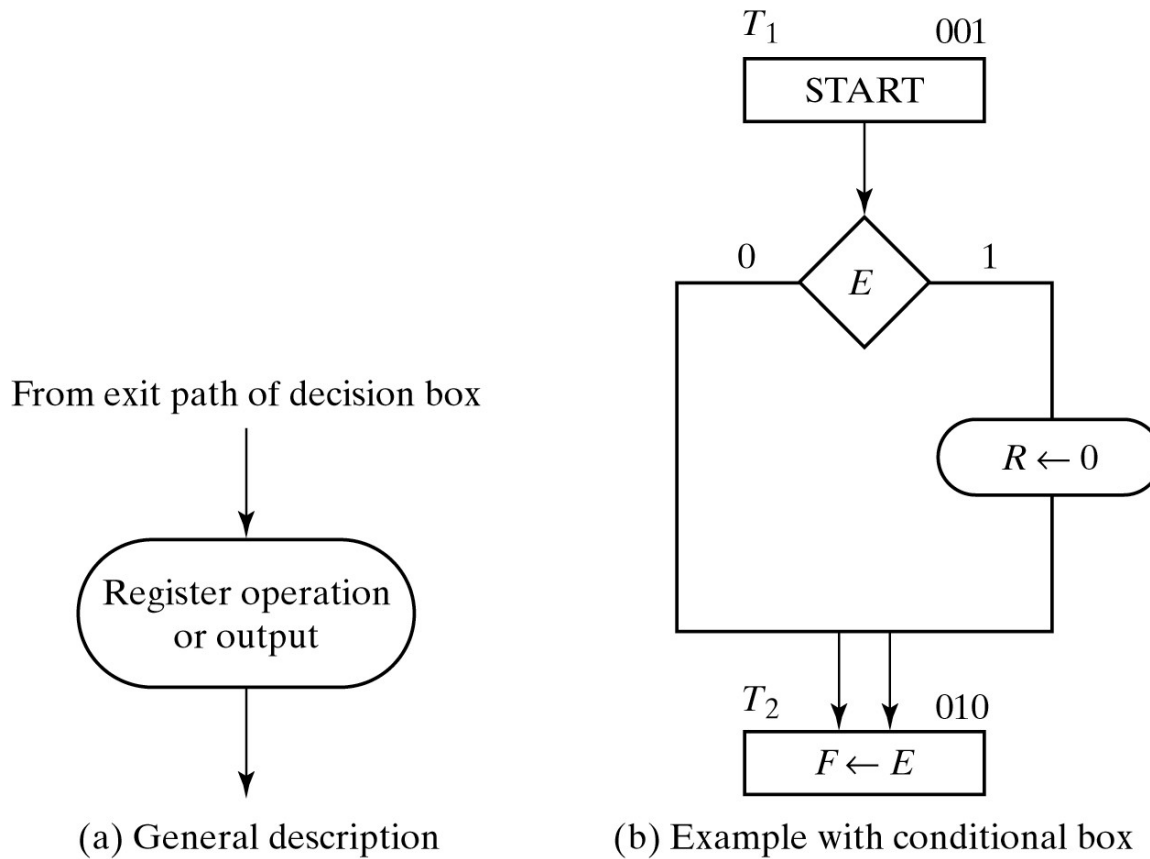


Fig. 8-5 Conditional Box

ASM Block

- It is not what happens to an author that cannot compose an ASM chart
- Represents a complete state
- Contains one state box
- And all associated decision and condition boxes

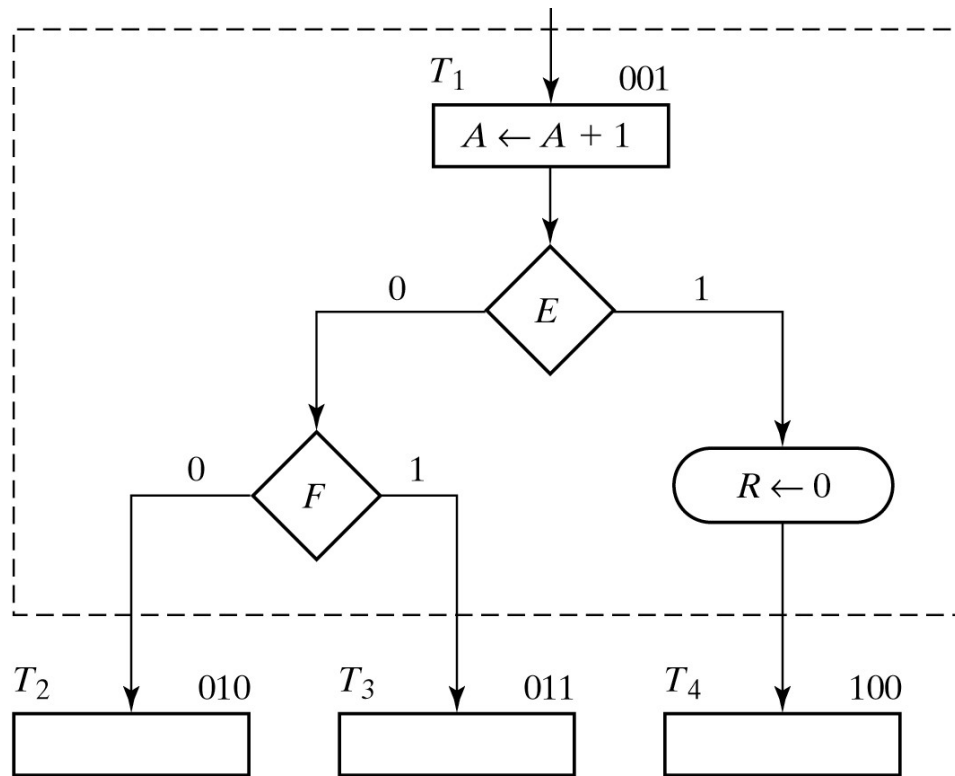


Fig. 8-6 ASM Block

State Diagram

- A state diagram does exactly the same as an ASM chart
- The ASM chart is better suited for real problems that may have more detail
- The diagram that follows does the same as the chart before

 


Fig. 8-7 State Diagram Equivalent to the ASM Chart of Fig. 8-6

Timing

- All F-F, both state F-F and registers are connected to a common clock and triggered in the same fashion.
- All operations within an ASM block take place at once, but the results are stored in the F-F at the clock edge

As a Result

- Max one assignment per F-F per ASM block
- The F-F do not change value in between clock edges
- A state is the time between the (triggering) clock edges

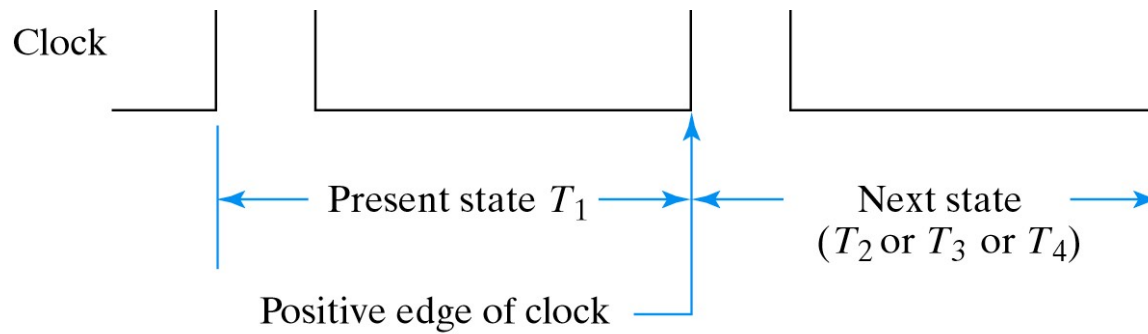


Fig. 8-8 Transition Between States

Design Example

- Design a sequential circuit that has
 - A counter: $A[4:1]$
 - Two F-F: E and F
 - An input S
- When the system is in the initial state and the input S becomes 1 the system goes in the counting state and F and A are reset

Design Example

- If the input S is 0 and the system is in the initial state, it remains in the initial state
- If in the counting state, E is set is $A[3]$ is 1, o/w reset
- If in the counting state, we go to the output state if $A[3:4] == 11$

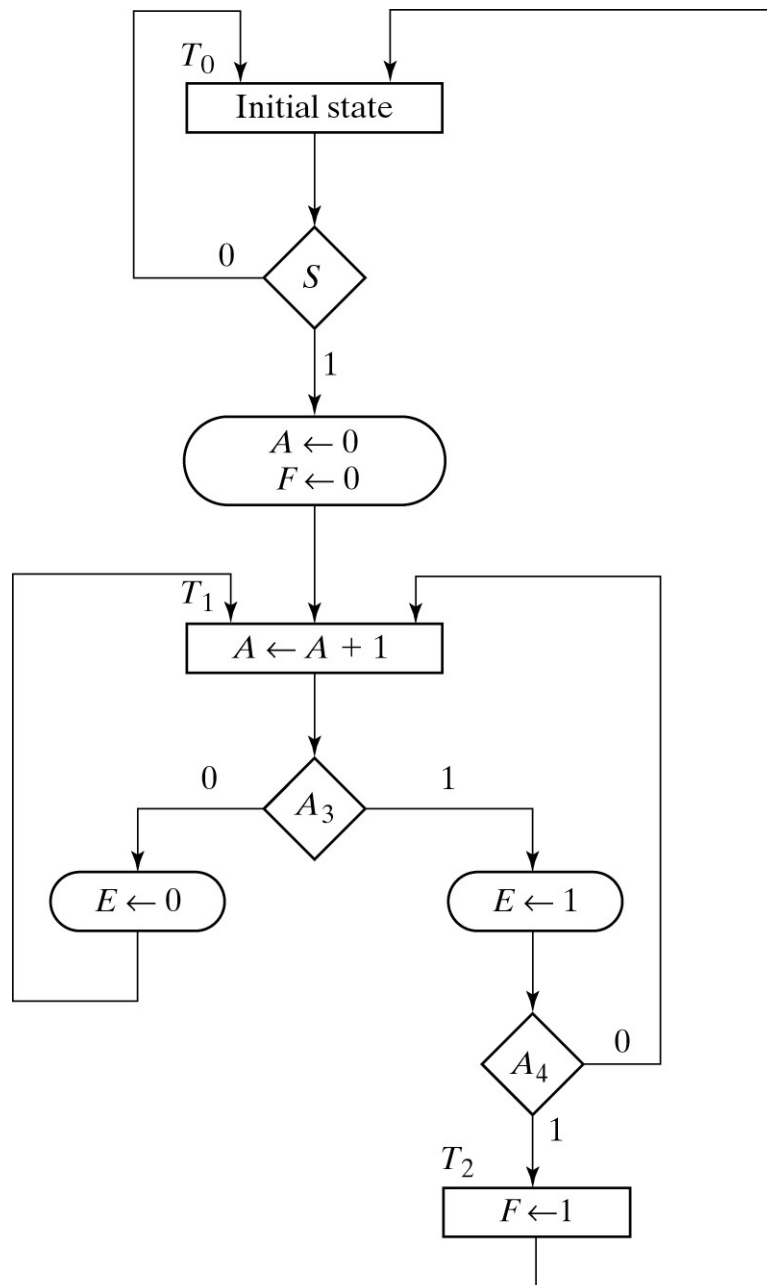


Fig. 8-9 ASM Chart for Design Example

Design the Datapath

- We can design it with state tables etc
- We can design it in an *ad hoc* fashion
 - This often the best

Assumptions

- We have:
 - A counter A with synchronous clear
 - Two flip-flops E and F of the J-K variety
 - An input S
- And also
 - The system has three inputs T0, T1, T2 that correspond to the three states

Let's Fry Some Bits

- The counter counts when in state T1
- The counter is reset when in state T0 and $S=1$

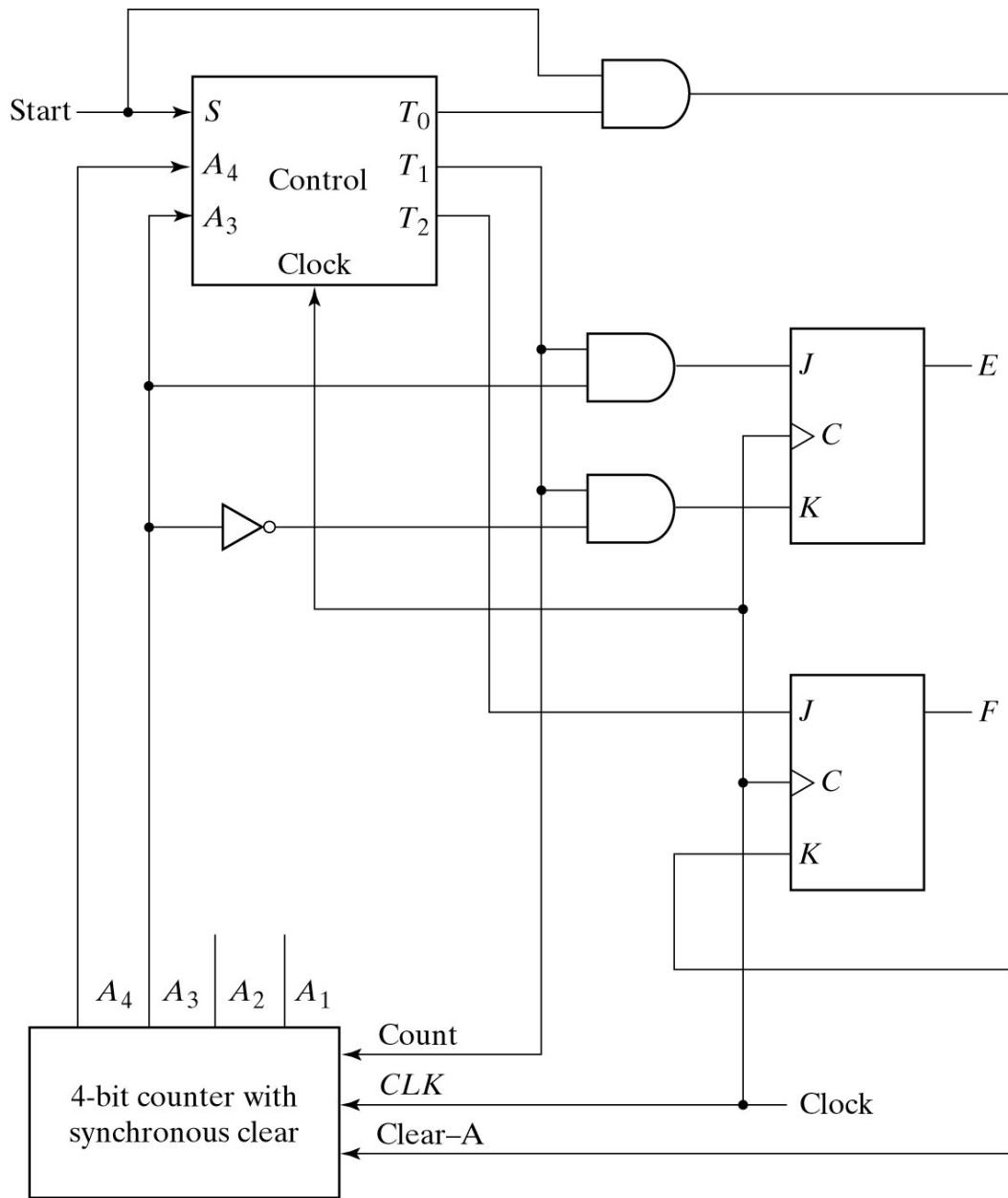


Fig. 8-10 Datapath for Design Example

Fry more Bits

- F-F E is set when in state T1 and A3=1
- F-F E is reset when in state T1 and A3=0
- F-F F is set when in state T2
- F-F F is reset when in state T0 and S=1

Control Logic


- We will see a few techniques to design the control logic
- There are many we will not see:
 - Either proprietary
 - Or historical

State Table

- We need the state table
- The state table can be big
- For this abysmally small example it has 32 entries
- We compress it

The Table

Present State		Inputs			Next State		Outputs		
G1	G0	S	A3	A4	G1	G0	T1	T2	T3
0	0	0	x	x	0	0	1	0	0
0	0	1	x	x	0	1	1	0	0
0	1	x	0	x	0	1	0	1	0
0	1	x	1	0	0	1	0	1	0
0	1	x	1	1	1	1	0	1	0
1	1	x	x	x	0	0	0	0	1

 

(a) State diagram for control

T_0 : if ($S = 1$) then $A \leftarrow 0, F \leftarrow 0$

T_1 : $A \leftarrow A + 1$

if ($A_3 = 1$) then $E \leftarrow 1$

if ($A_3 = 0$) then $E \leftarrow 0$

T_2 : $F \leftarrow 1$

(a) Register transfer operations

Fig. 8-11 Register Transfer Level Description of Design Example

The logic

- With a bit of symbolic manipulation
 - $D1 = G1' G0 A3 A4$
 - $D0 = G1' G0 + S G1' + G1 G0' + S G0'$
- And
 - $T0 = G1' G0'$
 - $T1 = G1' G0$
 - $T2 = G1 G0$

With Maps

- The F-F inputs are
 - $D1 = G1' G0 A3 A4$
 - $D0 = G1'G0 + G0'S$
- And the outputs are
 - $T0 = G0'$
 - $T1 = G1'G0$
 - $T2 = G1$

With Intuition

- The F-F inputs are:
 - $D1 = T1 A3 A4$
 - $D0 = T0 S + T1$
- And the outputs are
 - $T0 = G0'$
 - $T1 = G1'G0$
 - $T2 = G1$

 


Fig. 8-12 Logic Diagram of Control

With Verilog

- Behavioral description
 - the most abstract
 - h/w compiler is the king
- Structural description
 - we have to do the work
 - we give all the detail

The Preliminaries

```
module Example_RTL (S,CLK,Clr,E,F,A);  
//Specify inputs and outputs  
//See block diagram Fig. 8-10  
    input S,CLK,Clr;  
    output E,F;  
    output [4:1] A;  
//Specify system registers  
    reg [4:1] A;          //A register  
    reg E, F;           //E and F flip-flops  
    reg [1:0] pstate, nstate; //control register  
//Encode the states  
    parameter T0 = 2'b00, T1 = 2'b01, T2 = 2'b11;
```

The Control Section

```
//State transition for control logic
//See state diagram Fig. 8-11(a)
always @(posedge CLK or negedge Clr)
  if (~Clr) pstate = T0; //Initial state
  else pstate <= nstate; //Clocked operations
always @ (S or A or pstate)
  case (pstate)
    T0: if(S) nstate = T1;
    T1: if(A[3] & A[4]) nstate = T2;
    T2: nstate = T0;
    default: nstate = T0;
  endcase
```

The Register Transfer Logic

```
always @(posedge CLK)
  case (pstate)
    T0: if(S)
      begin
        A <= 4'b0000;
        F <= 1'b0;
      end
    T1:
      begin
        A <= A + 1'b1;
        if (A[3]) E <= 1'b1;
        else E <= 1'b0;
      end
    T2: F <= 1'b1;
  endcase
```

Multiplier

- An extremely useful thing
- An astonishingly complex thing to do if speed is important
- An outrageously tricky thing to do with floating point arithmetic

Back to Elementary School

- Let's multiply 23 by 19

- 10111
- x 10011
- -----
- 10111
- 10111
- 10111
- -----
- 110110101

Still in Elementary School

- The first number is called multiplicand
- The second is called multiplier
- The result is called product

Register Configuration

- We store the multiplicand in Reg. B
- We store the multiplier in Reg. Q
- Reg. Q will be shifted out to oblivion
- The product will be stored half in the accumulator A and half in Q

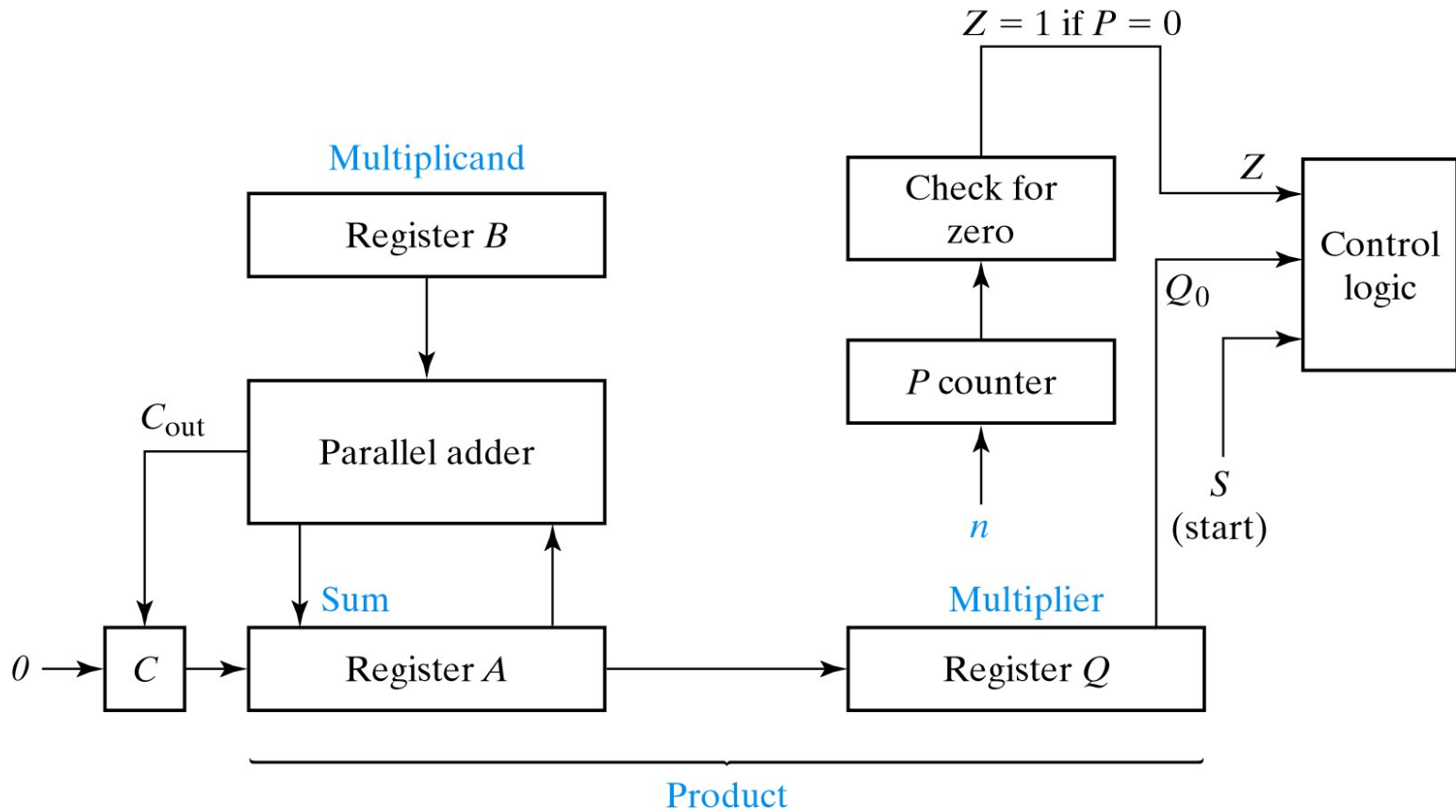


Fig. 8-13 Block Diagram of Binary Multiplier

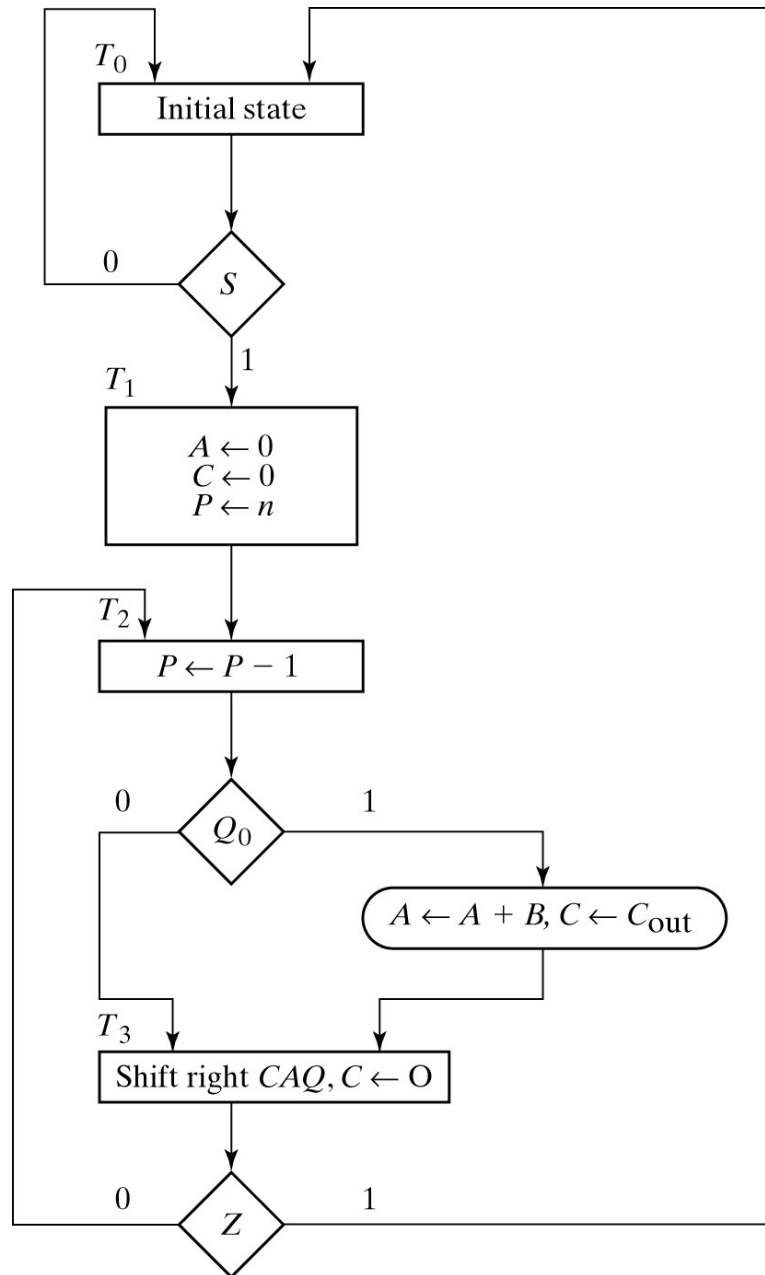



Fig. 8-14 ASM Chart for Binary Multiplier

Control Logic

- We have three choices
 - Binary
 - Gray Code
 - One-hot (1 F-F per state)
- We have three inputs:
 - S, Q0(?), Z

We know this stuff...

 - We can distill the ASM chart into a simple state diagram
- We do the tables
- Simplify
- And we are done



(a) State diagram

T_0 : Initial state

T_1 : $A \leftarrow 0, C \leftarrow 0, P \leftarrow n$

T_2 : $P \leftarrow P - 1$

if $(Q_0) = 1$ then $(A \leftarrow A + B, C \leftarrow C_{\text{out}})$

T_3 : shift right $CAQ, C \leftarrow 0$

(b) Register transfer operations

Fig. 8-15 Control Specifications for Binary Multiplier

How it looks like

- Q0 can be dealt with separately since it does not affect the sequence of states but only the commands to the datapath (e.g. the output of the control logic)

 


Fig. 8-16 Control Block Diagram

The Table

Present State		Input		Next State		Output			
G1	G0	S	Z	G1	G0	T0	T1	T2	T3
0	0	0	X	0	0	1	0	0	0
0	0	1	X	0	1	1	0	0	0
0	1	X	X	1	0	0	1	0	0
1	0	X	X	1	1	0	0	1	0
1	1	X	0	1	0	0	0	0	1
1	1	X	1	0	0	0	0	0	1

Simplify

- Assuming binary state assignment
 - $D1 = G1' G0 + G1 G0' + G1Z'$
 - $D0 = G1 G0' + G0'S$
- Assuming Gray state assignment
 - $D1 = G0 + G1Z'$
 - $D0 = G1 G0 + G1'G0'S$

Using the Outputs

- We need a decoder for this since there is not much minimization for the output circuits
- Plugging the outputs in
 - $D1 = T1 + T2 + T3Z'$
 - $D0 = T2 + T0 S$
- Does not matter if we use Gray or binary

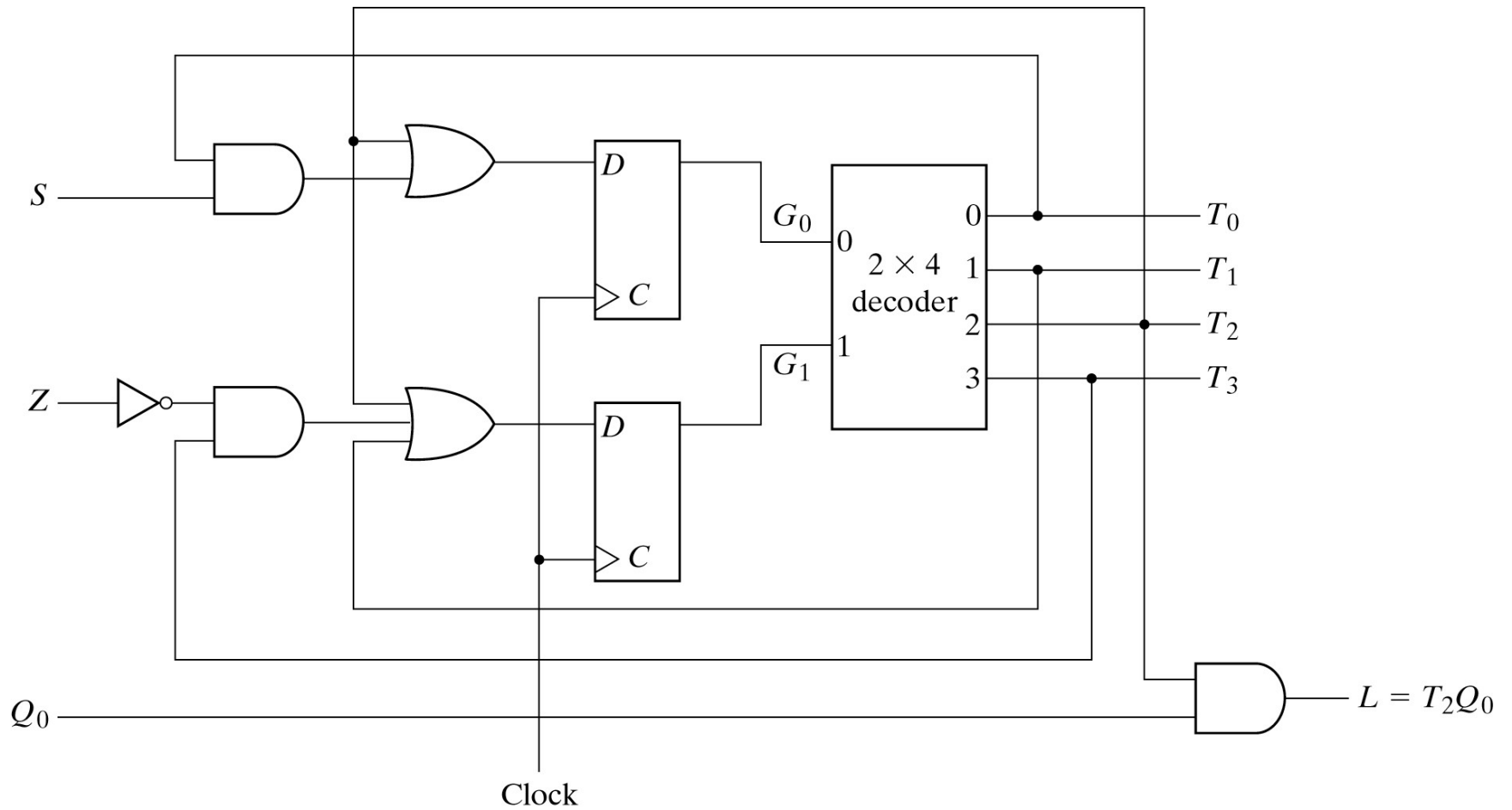


Fig. 8-17 Logic Diagram of Control for Binary Multiplier Using a Sequence Register and Decoder

Some Observations

- We cannot always avoid a full decoder
- Decoders need one gate per state
- Control logic does not always offer much of a chance for simplification

One F-F per State

- It is not always as costly as it looks
- Permits direct implementation from the ASM chart
- It makes sense!

 


Fig. 8-18 One Flip-Flop Per State Controller

HDL for Multiplier

```
module mltp(S,CLK,Clr,Binput,Qinput,C,A,Q,P);
  input S,CLK,Clr;
  input [4:0] Binput,Qinput;    //Data inputs
  output C;
  output [4:0] A,Q;
  output [2:0] P;
//System registers
  reg C;
  reg [4:0] A,Q,B;
  reg [2:0] P;
  reg [1:0] pstate, nstate;    //control register
  parameter T0=2'b00, T1=2'b01, T2=2'b10, T3=2'b11;
//Combinational circuit
  wire Z;
  assign Z = ~|P;              //Check for zero
```

State Transitions

```
always @(negedge CLK or negedge Clr)
  if (~Clr) pstate = T0;
  else pstate <= nstate;
always @(S or Z or pstate)
  case (pstate)
    T0: if (S) nstate = T1;
    T1: nstate = T2;
    T2: nstate = T3;
    T3: if (Z) nstate = T0;
        else nstate = T2;
  endcase
```

Register Transfer

```
always @(negedge CLK)
case (pstate)
T0: B <= Binput;          //Input multiplicand
T1: begin
    A <= 5'b00000;
    C <= 1'b0;
    P <= 3'b101;          //Initialize counter to n=5
    Q <= Qinput;         //Input multiplier
end
T2: begin
    P <= P - 3'b001;      //Decrement counter
    if (Q[0])
    {C,A} <= A + B;       //Add multiplicand
end
T3: begin
    C <= 1'b0;           //Clear C
    A <= {C,A[4:1]};      //Shift right A
    Q <= {A[0],Q[4:1]};   //Shift right Q
end
endcase
```

Design with MUX

- Allow us to minimize the number of components
- Quite simple to do.

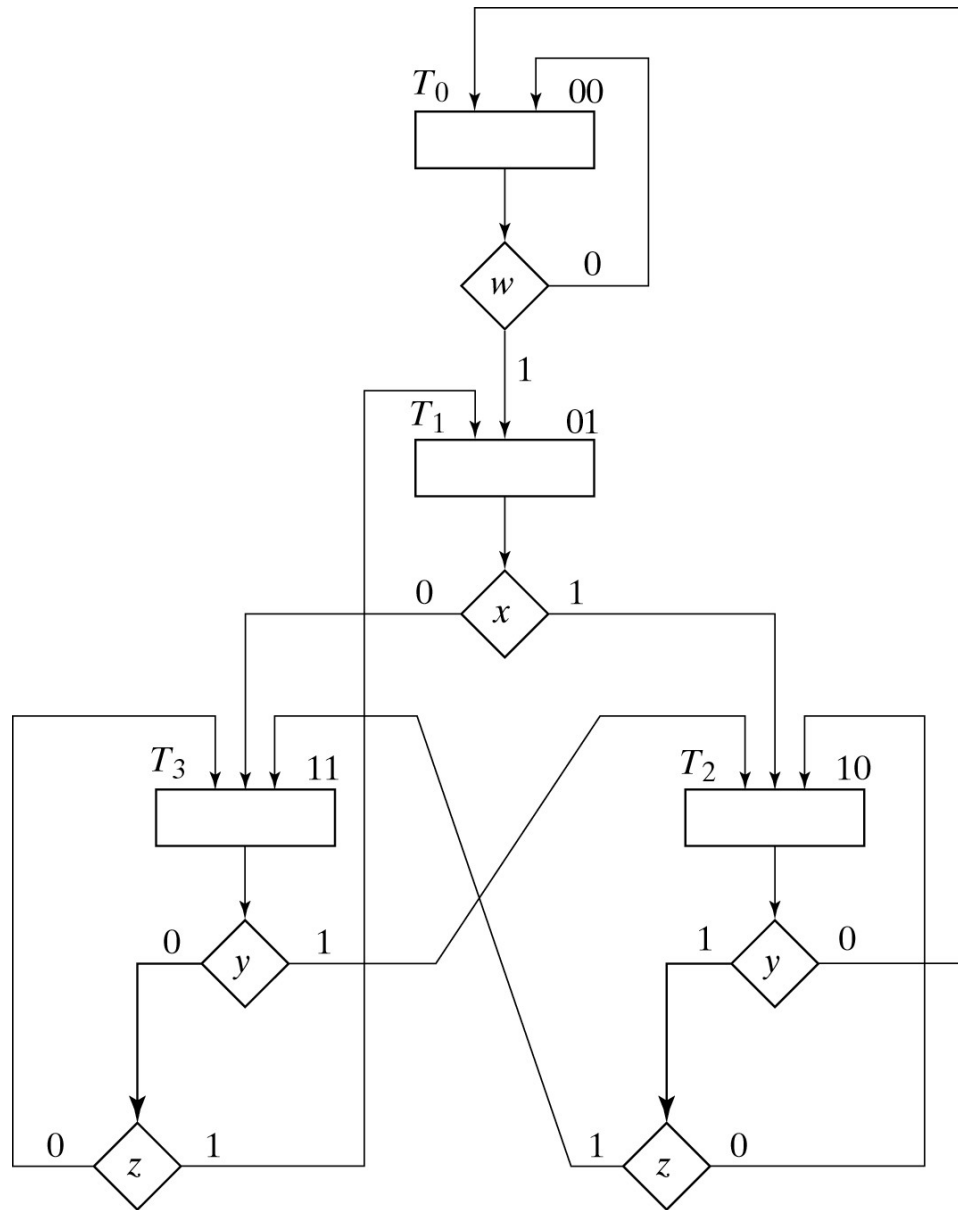


Fig. 8-19 Example of ASM Chart with Four Control Inputs

The Advantages

- MUXes allow us to break the combinational circuit in many simpler smaller ones
- Are among the few ways to design a 3 level combinational circuit
- Really useful when we have many variables and not all of them affect every state.

The Table

Present State	Next State	Input Conditions	MUX 1	MUX 2
G1 G0	G1 G0			
0 0	0 0	w'	0	w
0 0	0 1	w		
0 1	1 0	x	1	x'
0 1	1 1	x'		
1 0	0 0	y'	yz'+yz=y	yz
1 0	1 0	yz'		
1 0	1 1	yz		
1 1	0 1	y'z	y+y'z' = y+z'	y'
1 1	1 0	y		
1 1	1 1	y'z'		

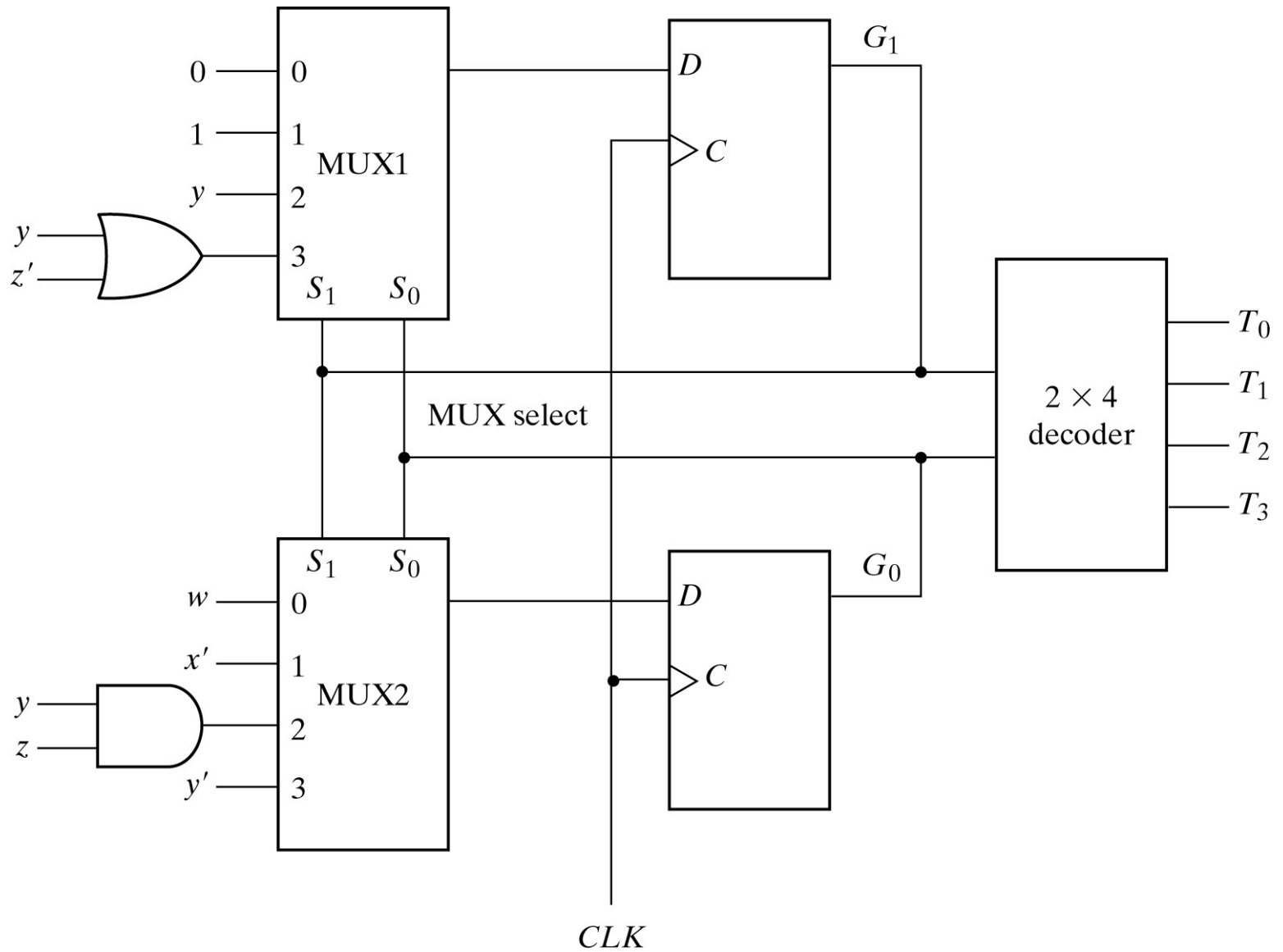


Fig. 8-20 Control Implementation with Multiplexers

With One-Hot

- We do this with the tried and true method (glare at the chart til your eyes get dry)
 - $T_0 = T_0 w' + T_2 y'$
 - $T_1 = T_0 w + T_3 y'z$
 - $T_2 = T_3 y + T_1 x + T_2 yz'$
 - $T_3 = T_3 y'z' + T_1 x' + T_2 yz$

Count the Ones

- Design a circuit that counts the ones in a register R1 and stores the result in counter R2
- The circuit keeps counting and shifting the contents of R1 out till R1 is all zeros
- R2 is initialized to all 1s.

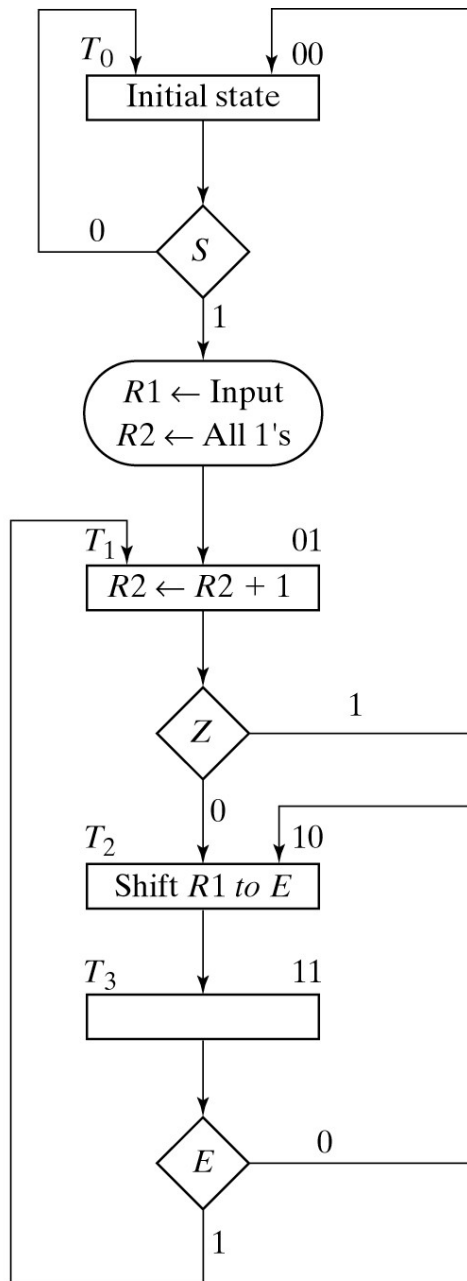


Fig. 8-21 ASM Chart for Count-of-Ones Circuit

We Also Need

- A F-F to store the bit shifted out of R1
- A combinational circuit to check if all bits of R1 are zero.

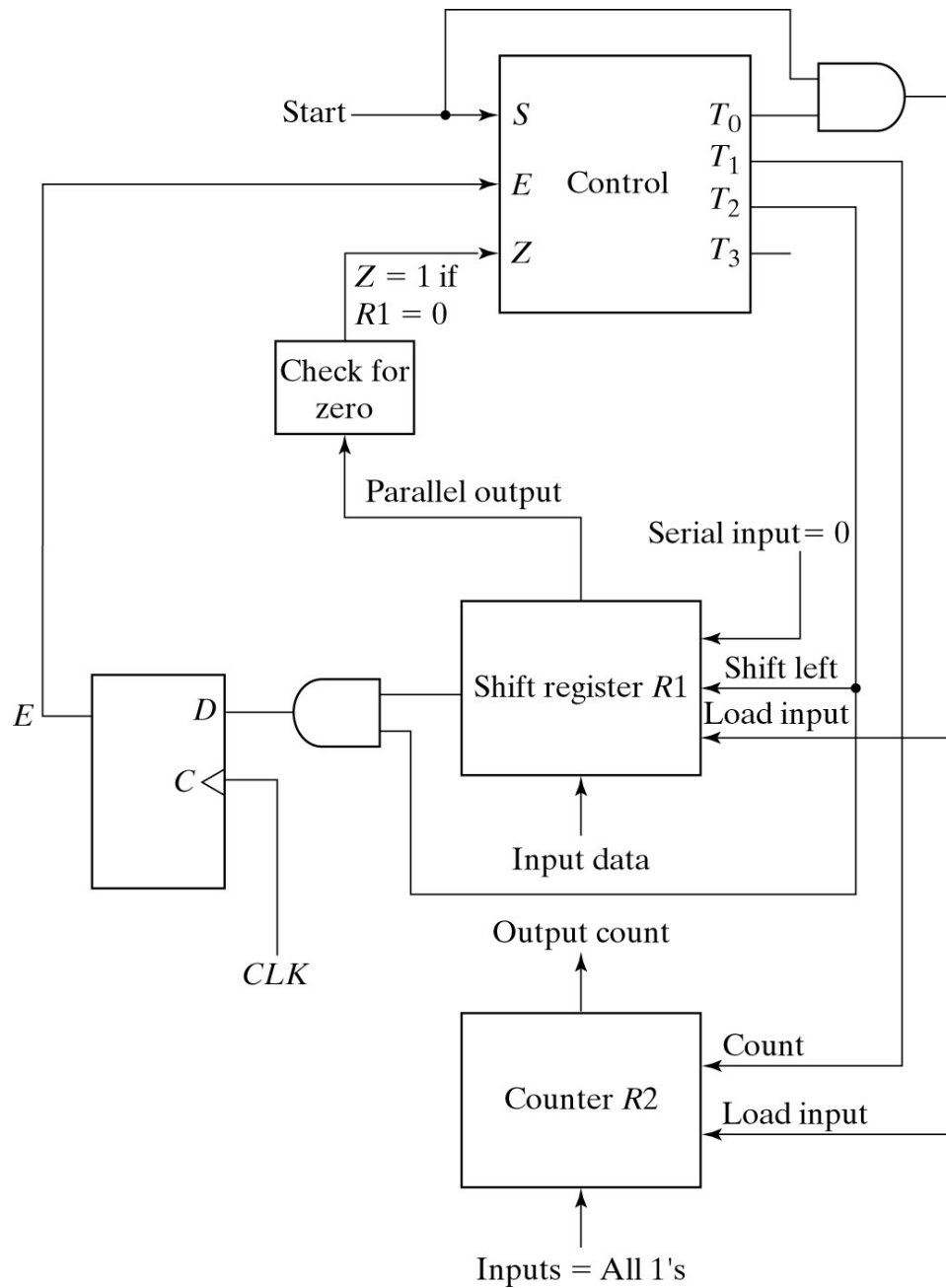


Fig. 8-22 Block Diagram for Count-of-Ones

The Table

Pr. St.		N. St.		Inp. Cond	MUX1	MUX2
G1	G0	G1	G0			
0	0	0	0	S'	0	S
0	0	0	1	S		
0	1	1	0	Z	1	Z'
0	1	1	1	Z'		
1	0	1	1	-	1	1
1	1	1	0	E'	E'	E
1	1	0	1	E		

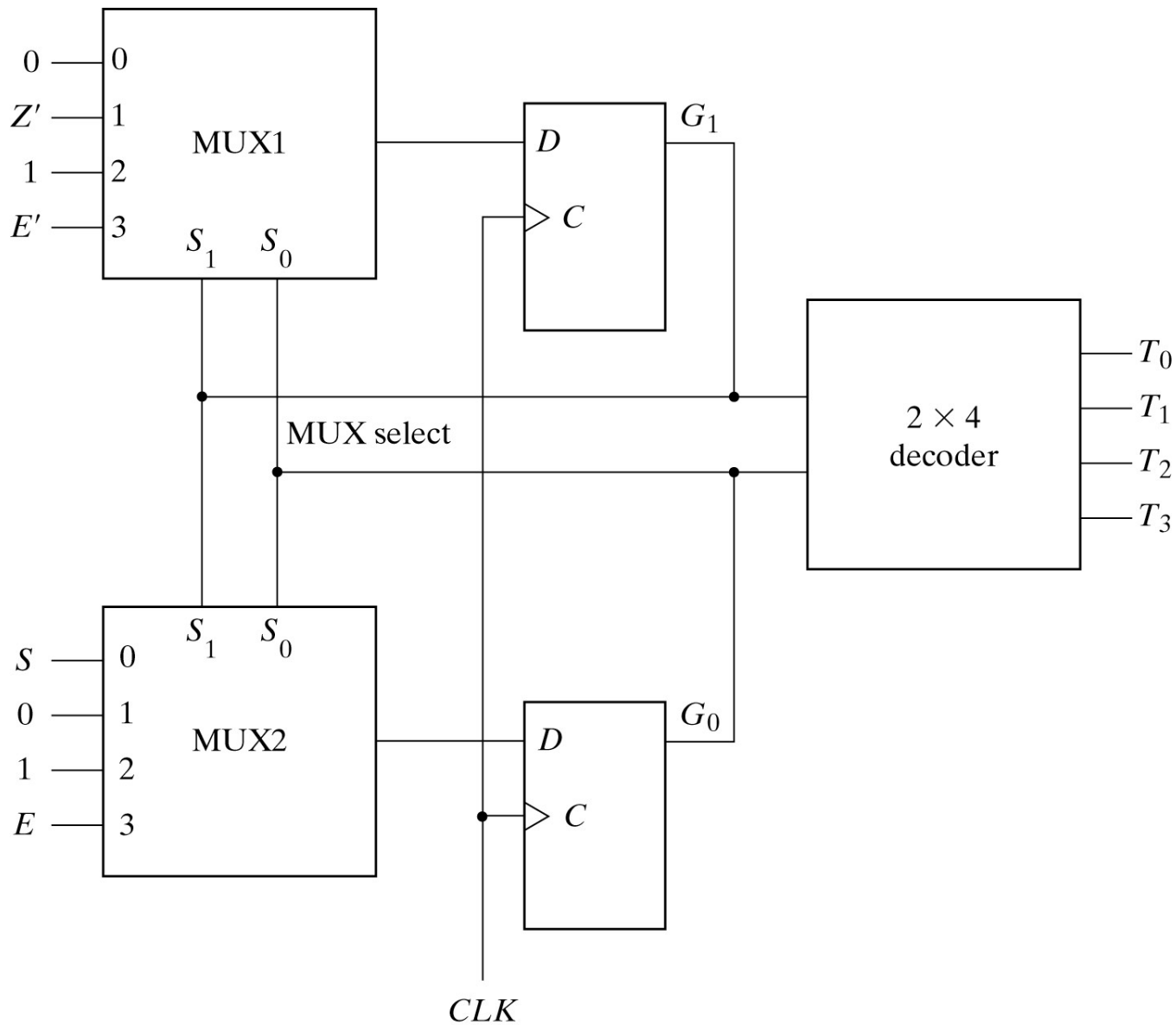


Fig. 8-23 Control Implementation for Count-of-Ones Circuit

 


Fig. P8-10 Control State Diagram for Problems 8-10 and 8-11

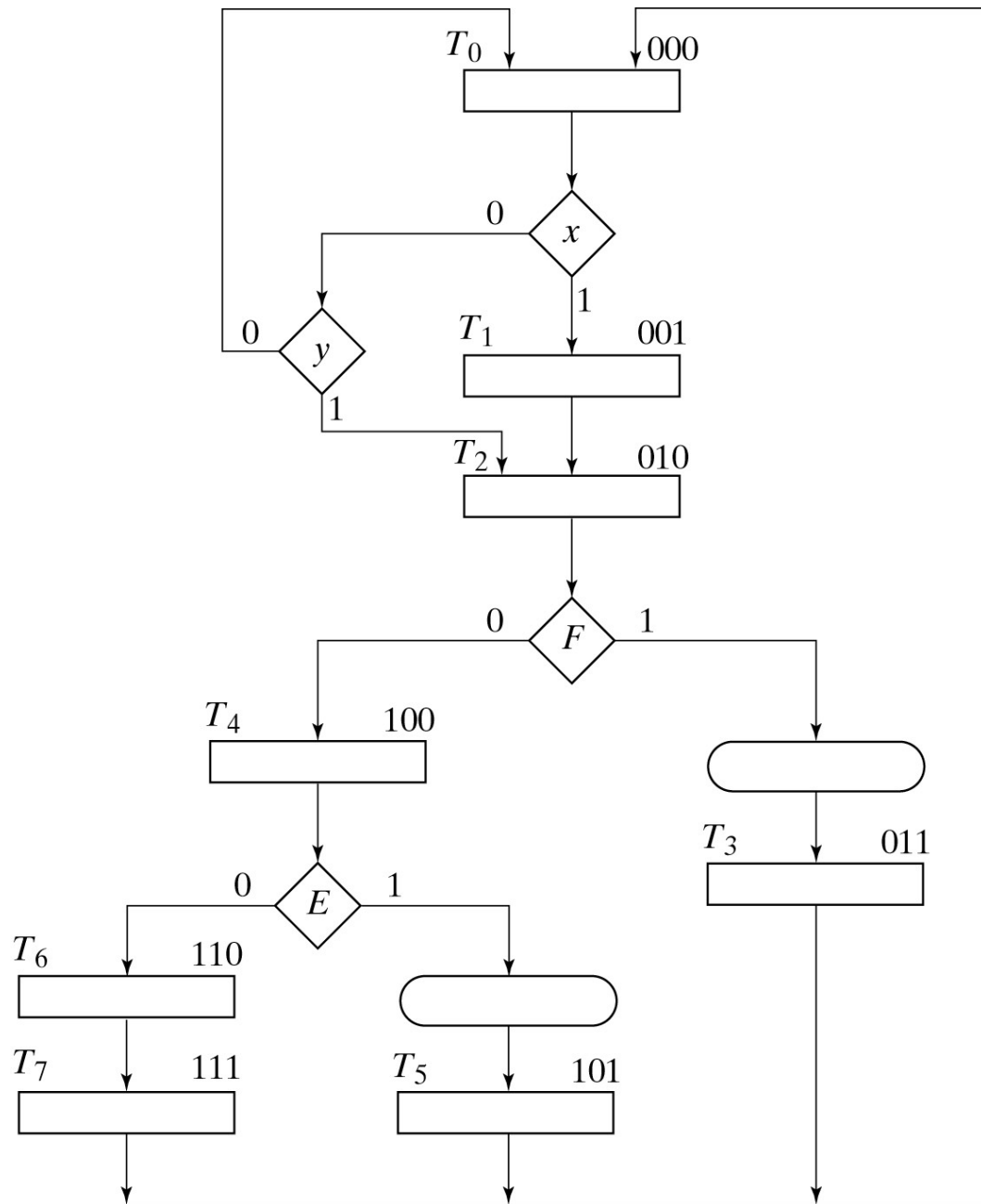


Fig. P8-20 ASM Chart for Problems 8-20